


- The terms of the canonical form which represents a particular truth table can be manipulated using the Boolean algebra so as to obtain a circuit having:
    - a minimum level (two level minimization)
    - or a minimum no of gates
    - or a minimum no of interconnections
  - The possibility of proving that a particular form of a reduced expression is truly a minimum is considered.
-

For  $n$  inputs or literals,  
the truth table has  $2^n$  rows.

If  $Q = 1$  for  $m$  of the  $2^n$  rows,  
we require  $m$   $n$ -input AND gates and  
1  $m$ -input OR gate for Sum of Products.

---

<i>A</i>	<i>B</i>	<i>C</i>	<i>Q</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

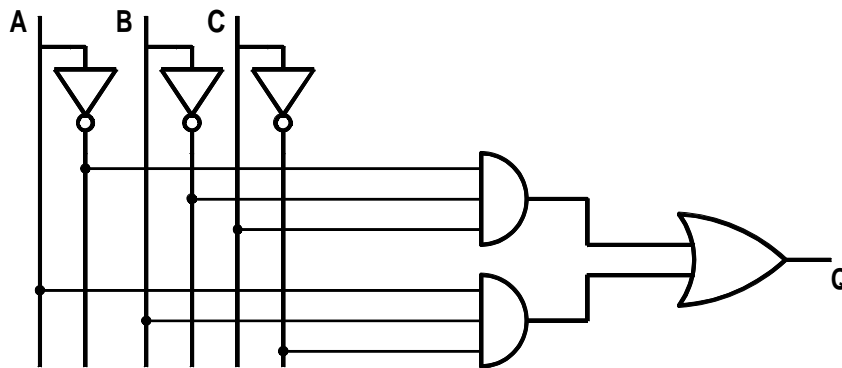

Truth table for  $Q = \overline{A}BC + A\overline{B}C$   
and the Sum of Products circuit.

---

Ideally we would be able to combine rows of the truth table and reduce the logic gate count and also the track count.

There are a number of ways of doing this which are all based ultimately on Boolean minimization.

To be discussed in next five units.

---

Main tools for Boolean Minimization.

$$A + \bar{A} = 1$$

and T3

$$A + AB = A \quad A(A + B) = A$$

and T4

$$A + \bar{A}.B = A + B \quad A(\bar{A} + B) = A.B$$

---

Simplify the following canonical expression to a Sum of Products.

$$Q = A.B.C + A.B.\bar{C} + \bar{A}.B.C$$

Use  $A + \bar{A} = 1$ .

$$\begin{aligned} Q &= A.B.C + A.B.\bar{C} + \bar{A}.B.C \\ &= A.B.(C + \bar{C}) + \bar{A}.B.C \\ &= A.B.1 + \bar{A}.B.C \\ &= A.B + \bar{A}.B.C \end{aligned}$$

Sum of Products, as required.

---

The simplification is not always unique.

$$\begin{aligned} Q &= A.B.C + A.B.\bar{C} + \bar{A}.B.C \\ &= A.B.C + \bar{A}.B.C + A.B.\bar{C} \\ &= (A + \bar{A}).B.C + A.B.\bar{C} \\ &= B.C + A.B.\bar{C} \end{aligned}$$

This is just as simple  
but is different from

$$Q = A.B + \bar{A}.B.C$$

It is not possible to prove that the simplest  
form has been found.

---

Convert to the minterm list form.

Simplify the expression, using Boolean algebra

Draw the circuit.

$$Q = \overline{A}.\overline{B}.\overline{C}.\overline{D} + \overline{A}.\overline{B}.C.D + \overline{A}.B.C.D + A.\overline{B}.\overline{C}.\overline{D} \\ + A.\overline{B}.C.\overline{D} + A.\overline{B}.C.D + A.B.C.\overline{D} + A.B.C.D$$

Convert the literals to binary,

Convert the binary number to decimal and obtain the minterm list directly.

$$Q = \sum m(0000, 0011, 0111, 1000, \\ 1010, 1011, 1110, 1111) \\ = \sum m(0, 3, 7, 8, 10, 11, 14, 15)$$

---



Convert to the minterm list form.

Simplify the expression, using Boolean algebra

Draw the circuit.

A Boolean simplification proceeds as follows:


$$\begin{aligned} Q &= \overline{A}.\overline{B}.\overline{C}.\overline{D} + \overline{A}.\overline{B}.C.D + \overline{A}.B.C.D + A.\overline{B}.\overline{C}.\overline{D} \\ &\quad + A.\overline{B}.C.\overline{D} + A.\overline{B}.C.D + A.B.C.\overline{D} + A.B.C.D \\ &= (\overline{A} + A).\overline{B}.\overline{C}.\overline{D} + \overline{A}.(B + \overline{B}).C.D \\ &\quad + A.\overline{B}.C(\overline{D} + D) + A.B.C.(\overline{D} + D) \\ &= \overline{B}.\overline{C}.\overline{D} + \overline{A}.C.D + A.\overline{B}.C + A.B.C \\ &= \overline{B}.\overline{C}.\overline{D} + \overline{A}.C.D + A.C.(B + \overline{B}) \\ &= \overline{B}.\overline{C}.\overline{D} + \overline{A}.C.D + A.C \\ &= \overline{B}.\overline{C}.\overline{D} + C(\overline{A}.D + A) \\ &= \overline{B}.\overline{C}.\overline{D} + C(D + A) \text{ by T4} \\ &= \overline{B}.\overline{C}.\overline{D} + C.D + A.C \end{aligned}$$

---

Convert to the minterm list form.

Simplify the expression, using Boolean algebra

Draw the circuit.

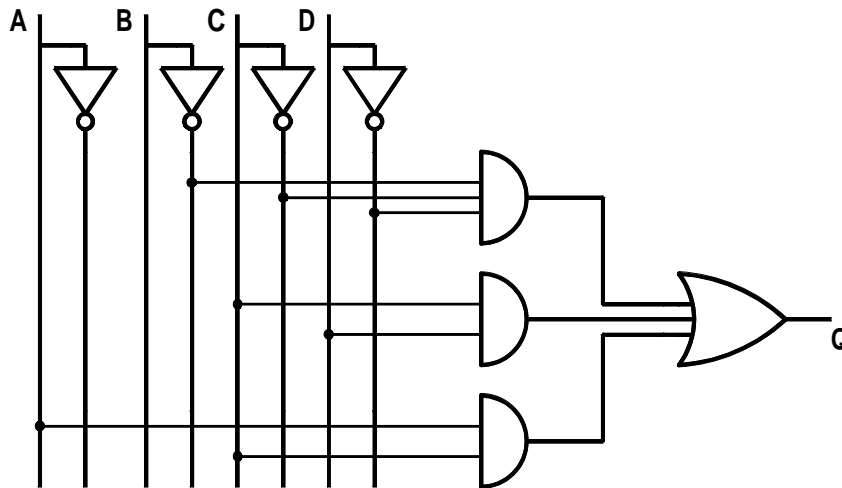

$$\begin{aligned}
 Q &= \overline{A}.\overline{B}.\overline{C}.\overline{D} + \overline{A}.\overline{B}.C.D + \overline{A}.B.C.D + A.\overline{B}.\overline{C}.\overline{D} \\
 &\quad + A.\overline{B}.C.\overline{D} + A.\overline{B}.C.D + A.B.C.\overline{D} + A.B.C.D \\
 &= \overline{B}.\overline{C}.\overline{D} + C.D + A.C
 \end{aligned}$$

1. Simplify the following expression

$$F1 = ABC\bar{C} + A\bar{B}\bar{C} + \bar{A}BC + \bar{A}BC$$

2. Simplify the following expression

$$F2 = ABC\bar{C} + \bar{A}BC + ABC$$

3. Simplify the following expression

$$F3 = \bar{A}BC\bar{C} + ABC\bar{C} + \bar{A}BC + A\bar{B}C$$

---

1. Simplify the following expression

$$F4 = \overline{ABCD} + \overline{A}BCD + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} \\ + A\overline{B}CD + \overline{A}B\overline{C}D + ABCD + A\overline{B}C\overline{D}$$

2. Show, by use of the postulates and theorems of Boolean algebra and by direct calculation using a truth table, that the following identity is true.

$$F5 = C.B + A.\overline{B}.C.D + C.\overline{D} \\ + A.\overline{C} + \overline{A}.B.\overline{C} + \overline{A}.\overline{B}.\overline{C}.\overline{D} \\ = = A + B + \overline{D}$$

Draw the logic gate diagram which represents each side of the identity.

---