


- A function such as $Q = A \oplus B \oplus C \oplus D$ will only take logic 1 when an odd number of A , B , C and D have logic 1. The function therefore acts as a parity generator.
 - An n input Sum-of-Products function requires 2^n sets of test inputs.
An n input Reed-Muller circuit can be tested using $4 + n + 2n_e$ sets of test inputs
-


- Reed-Muller expressions are minimized by selecting either the uncomplemented or complemented form of each of the inputs so as to obtain a minimized expression.
 - The Polarity Vector is used to define which form of the input is to be used in the Reed-Muller expression.
 - The techniques for minimizing Reed-Muller expressions are the subject of ongoing research.
-

- A Sum of Products expression of n variables has 2^n rows in truth table.
 - Therefore 2^n tests must be carried out to verify that system is operating correctly.
 - Possible for prototype but not for production.
 - Use batch statistics for quality control.
 - Or change to Reed-Muller Logic.
-

$$f(x_4, x_3, x_2, x_1, x_0) = x_1x_2 \oplus x_1x_3 \oplus x_1x_4 \oplus x_3x_4 \oplus x_1x_2x_3 \oplus x_2x_3x_4 \oplus x_0$$

is implemented by

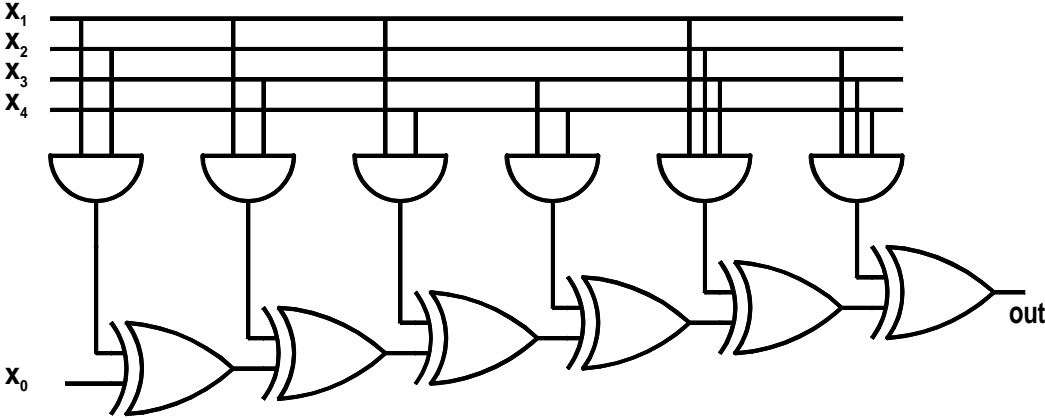


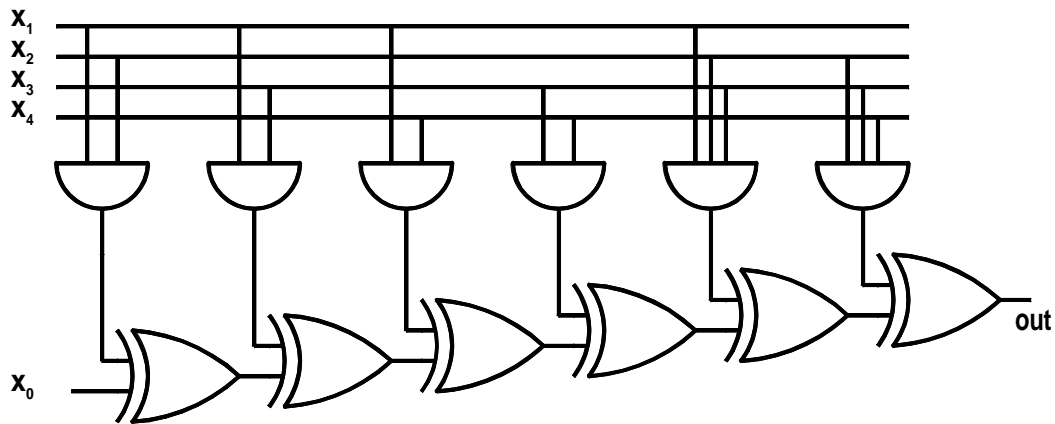

Test vector

x_0	x_1	x_2	x_3	x_4	out
0	1	1	1	1	0

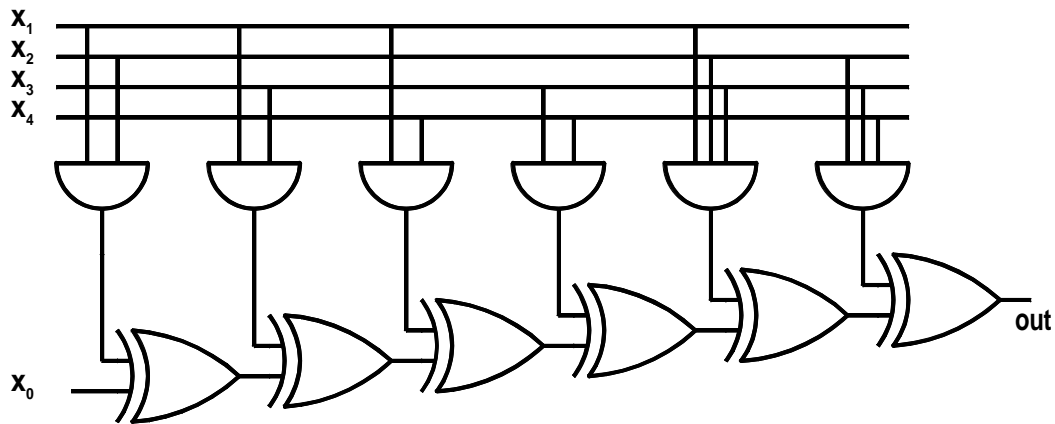
Verifies that all AND gates can give 1 out
and
that XOR cascade operates



Test vector


$$\begin{array}{cccccc} & x_0 & x_1 & x_2 & x_3 & x_4 & \text{out} \\ (& 0 & 0 & 0 & 0 & 0 & 0 &) \end{array}$$

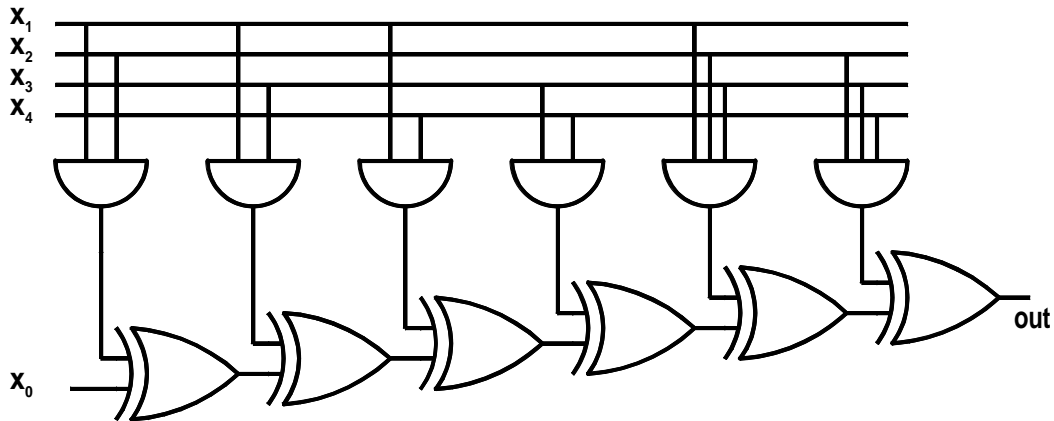Verifies that all AND gates can give 0 out
and
that XOR cascade operates



$$F_C = \begin{pmatrix} 0 & 1 & 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & 1 & 1 & 1 & 1 & 1 \\ 1 & 0 & 0 & 0 & 0 & 1 \end{pmatrix}$$

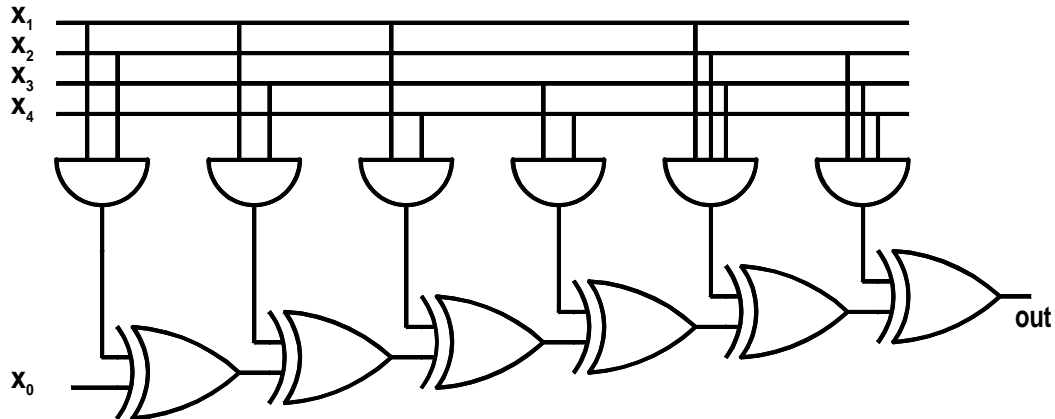
Tests all AND gates and ALL XOR gates.
No Stuck-at-0 or Stuck-at-1 gates.



Are all AND gates connected to inputs?

$$F_A = \begin{pmatrix} 0 & 0 & 1 & 1 & 1 & 0 \\ 0 & 1 & 0 & 1 & 1 & 1 \\ 0 & 1 & 1 & 0 & 1 & 0 \\ 0 & 1 & 1 & 1 & 0 & 1 \end{pmatrix}$$

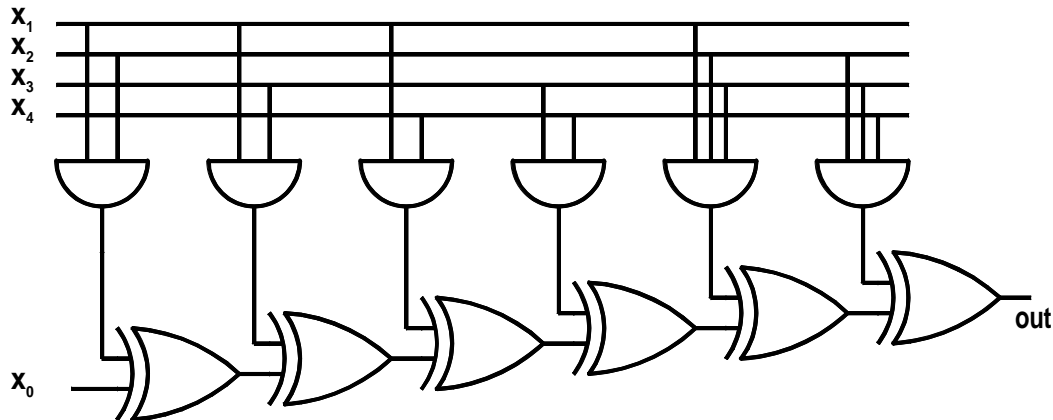Faulty input line connected to EVEN number of AND gates not detected in this test.



Test for faults on input lines connected to EVEN number of AND gates with

$$\mathbf{F}_{E1} = \begin{pmatrix} 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & 0 & 1 \end{pmatrix}$$

Similar test matrices are needed for each of the other inputs which also appear in an even number of product terms, so if there are n_e such input terms then there will be $2n_e$

The total number of tests which have to be carried out on a Reed-Muller AND/XOR type of gate array in order to test for correct functioning is therefore $4 + n + 2n_e$ with the one restriction that only single s-a-1 or s-a-0 type faults occur.

We therefore see that the number of tests required for testing AND/XOR gate arrays is a simple linear function of the number of primary inputs whereas the number on tests required to test an AND/OR Boolean type circuit is of the order of 2^n .

- We only used uncomplemented forms x_1, A etc.
 - It is possible to use complemented forms $\overline{x_1}, \overline{A}$, etc.
 - Keep track of which Polarity is being used with Polarity Vector.
 - A, B, C, D has Polarity Vector $\mathbf{k} = (1, 1, 1, 1)$
 - $A, \overline{B}, \overline{C}, D$ has Polarity vector $\mathbf{k} = (1, 0, 0, 1)$
-

To convert expression from form having Polarity vector $\mathbf{k} = (1, 1, 1, 1)$

to form having Polarity vector $\mathbf{k} = (1, 0, 0, 1)$

use the substitutions $x_1 = 1 \oplus \overline{x_1}$

and $x_2 = 1 \oplus \overline{x_2}$

and multiply out

For example a typical conversion to form having polarity vector $\mathbf{k} = (1, 0, 0, 1)$ might be:

$$\begin{aligned}
 & f(x_4, x_3, x_2, x_1) \\
 = & x_0 \oplus x_1(1 \oplus \overline{x_2}) \oplus x_1(1 \oplus \overline{x_3}) \oplus x_1x_4 \oplus (1 \oplus \overline{x_3})x_4 \\
 & \oplus x_1(1 \oplus \overline{x_2})(1 \oplus \overline{x_3}) \oplus (1 \oplus \overline{x_2})(1 \oplus \overline{x_3})x_4 \\
 = & x_0 \oplus x_1 \oplus x_1\overline{x_2} \oplus x_1 \oplus x_1\overline{x_3} \oplus x_1x_4 \oplus x_4 \oplus \overline{x_3}x_4 \\
 & \oplus x_1 \oplus x_1\overline{x_2} \oplus x_1\overline{x_3} \oplus x_1\overline{x_2x_3} \oplus x_4 \oplus \overline{x_2}x_4 \oplus \overline{x_3}x_4 \oplus \\
 = & x_0 \oplus (x_1 \oplus x_1 \oplus x_1) \oplus (x_4 \oplus x_4) \oplus (x_1\overline{x_2} \oplus x_1\overline{x_2}) \oplus \\
 & \oplus x_1\overline{x_3}) \oplus x_1x_4 \oplus \overline{x_2}x_4 \oplus (\overline{x_3}x_4 \oplus \overline{x_3}x_4) \oplus x_1\overline{x_2x_3} \oplus \\
 = & x_0 \oplus x_1 \oplus 0 \oplus 0 \oplus 0 \oplus 0 \oplus x_1x_4 \oplus \overline{x_2}x_4 \oplus 0 \oplus x_1\overline{x_2x_3} \\
 = & x_0 \oplus x_1 \oplus 0 \oplus x_1x_4 \oplus \overline{x_2}x_4 \oplus x_1\overline{x_2x_3} \oplus \overline{x_2x_3}x_4
 \end{aligned}$$