 






- Base 2 binary counters can be used to construct base  $m$  counters by a Clear instruction when the modulus is reached.
  - A Down counter counts down from an initial binary number when the  $\overline{Q}$  output of the binary counters is used for inter-stage transfer.
  - The count ripples through asynchronous counters.
  - All of the stages of a synchronous counter change state at the same time.
-




### Modulo 10 Counter.

When the output  $Z = 1001$  is reached  
next count gives the output  $Z_{10} = 1010$   
NAND gates generate a reset to zero

---

    

 **(a) 3 bit up counter. (b) 3 bit down counter.**




### **Switchable 3 bit up/down counter.**

The u/d input allows the direction of count to be switched as required.

The AND/OR gates select the signals applied to the clock inputs from either the  $Q$  or the  $\overline{Q}$  outputs from the flip flops.

---

 

### **Synchronous counter and counting waveforms.**

All of the outputs change state simultaneously

Avoids readout problems at the expense of increased circuit complexity.

Incoming count pulse fed to all binary counter stages simultaneously.