

When resistors are connected in series, the same current flows in all of the resistors.

The voltage drop across the equivalent resistor R_{series} is:-

$$V_{series} = IR_{series} = IR_1 + IR_2 + IR_3 + \dots$$

Therefore $R_{series} = R_1 + R_2 + R_3 + \dots$

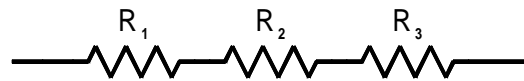


Figure 2.1:—

Example 1

Calculate the current in the circuit of Figure 2.2, if the voltage across the two resistors in series is $3.8V$.

Calculate the current in the $100R$ resistor.

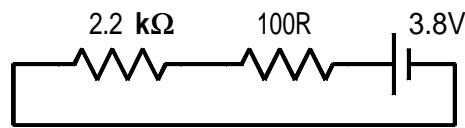


Figure 2.2:—

$$\begin{aligned} R_s &= R_1 + R_2 = 2.2k + 100 \\ &= 2.2 \times 10^3 + 100 = 2300\Omega \\ I &= \frac{3.8V}{2300\Omega} \\ &= 1.65 \times 10^{-3} = 1.65mA \end{aligned}$$

Example 2.

Calculate the current in the circuit of Figure 2.3, if the voltage across the $1.8k\Omega$ resistor is $6.4V$. Calculate the voltage across the $2.7k\Omega$ resistor. Calculate the battery voltage.

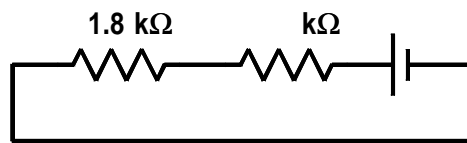


Figure 2.3:—

$$\begin{aligned}\text{Current} &= I = \frac{6.4V}{1.8k\Omega} = \frac{6.4}{1800} \\ &= 3.55 \times 10^{-3} = 3.55mA\end{aligned}$$

$$\begin{aligned}V_{2.7k\Omega} &= 3.55mA \times 2.7k\Omega \\ &= 3.55 \times 10^{-3} \times 2.7 \times 10^3 = 9.58V\end{aligned}$$

$$V_{\text{Battery}} = 6.4V + 9.6V = 16V$$
