

When resistors are connected in parallel, the same voltage difference or potential difference is present across all of the resistors.

$$V_p = I_{Total}R_p = I_1R_1 = I_2R_2 = I_3R_3 = \dots$$

$$\text{but } I_{Total} = I_1 + I_2 + I_3 + \dots$$

$$\text{Therefore } \frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

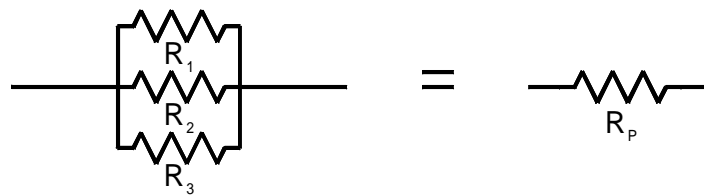


Figure 3.1:—

---

## Example 1

Calculate the equivalent resistance for the parallel resistor circuit shown in the Figure 3.2.

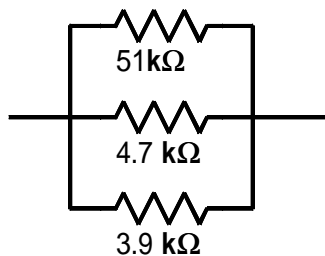


Figure 3.2:—

$$\begin{aligned}\frac{1}{R_p} &= \frac{1}{51k\Omega} + \frac{1}{4.7k\Omega} + \frac{1}{3.9k\Omega} \\ &= 4.89 \times 10^{-4} \Omega^{-1}\end{aligned}$$

Therefore

$$\begin{aligned}R_p &= 2046\Omega \\ &= 2.046k\Omega\end{aligned}$$

---

## Example 2

In the circuit shown in Figure 3.3, if the current in the  $820\Omega$  resistor is measured to be  $2.5\text{mA}$ , calculate the battery voltage and also calculate the total current flowing through the battery. Calculate the current in the  $3.9\text{k}\Omega$  resistor.


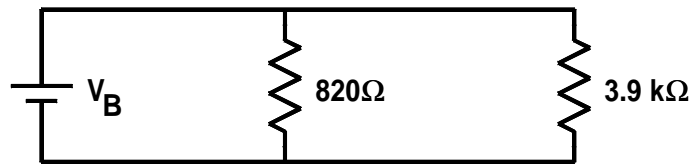


Figure 3.3:—

---

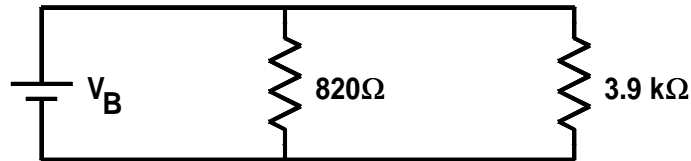

$$\begin{aligned}
 V_{Battery} &= 2.5\text{mA} \times 820\Omega \\
 &= 2.5 \times 10^{-3} \times 820\text{V} \\
 &= 2.05\text{V}
 \end{aligned}$$

$$\begin{aligned}
 \frac{1}{R_p} &= \frac{1}{820} + \frac{1}{3900} \\
 &= 1.48 \times 10^{-3}
 \end{aligned}$$

Therefore  $R_p = 677\Omega$

$$\begin{aligned}
 \text{Hence } I_{Total} &= \frac{2.05\text{V}}{677\Omega} \\
 &= 3.03 \times 10^{-3}\text{A} \\
 &= 3.03\text{mA}
 \end{aligned}$$

$$\begin{aligned}
 \text{and } I_{3.9\text{k}\Omega} &= \frac{2.05\text{V}}{3.9 \times 10^3\Omega} \\
 &= 5.26 \times 10^{-4}\text{A} \\
 &= 0.526\text{mA} \quad \text{or} \quad 526\mu\text{A}
 \end{aligned}$$


---