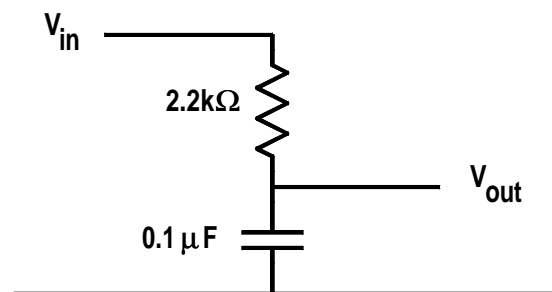



For a first order filter, RC or RL, the Corner Frequency,  $f_c$ , in Hertz is given by:–

$$f_c = \frac{1}{2\pi CR} \quad \text{or} \quad \frac{R}{2\pi L}$$

On a dB versus log frequency plot, the filter response is approximated by two straight lines, one of slope 0 and the other of slope -20dB per decade and drawn through the point at the corner frequency and 0dB ( $\log f_c$ , 0dB).

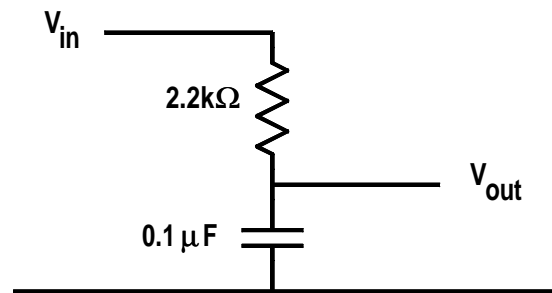At the corner frequency the attenuation is -3dB and the phase shift is  $\frac{\pi}{4}$  or 45 degrees.






Calculate the frequency response by repeating the calculations of Example 15.1 for a range of frequencies.

The response in decibels, dB, as a function of the log of the frequency, is plotted and a response curve such as that in Figure 16.2 is obtained.

---

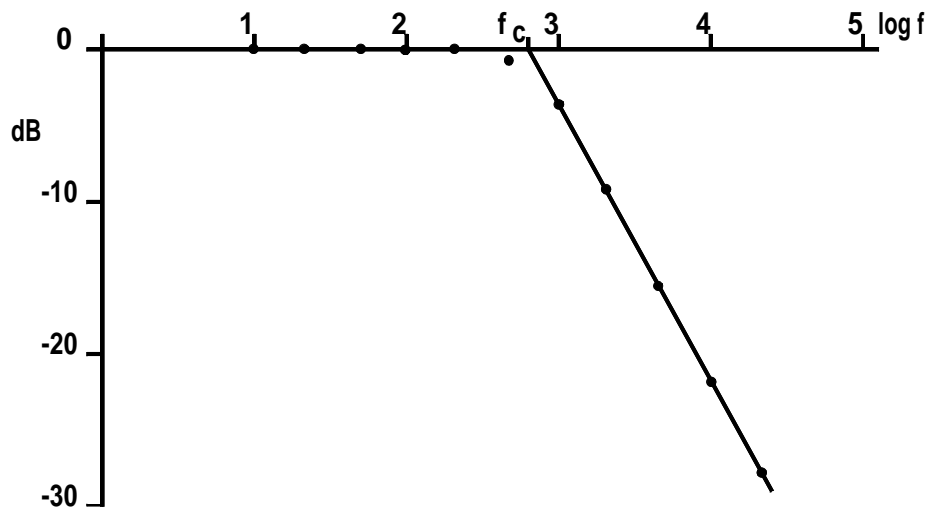


Use frequencies 10, 20, 50, 100, 200, 500, 1000, 2000, 5000, 10000 Hz and the resulting points are shown on the plot.

The sequence 1, 2, 5 and multiples of 10 give roughly equally spaced points on a log frequency plot.

In the laboratory you should try to use these multiples where possible.

---

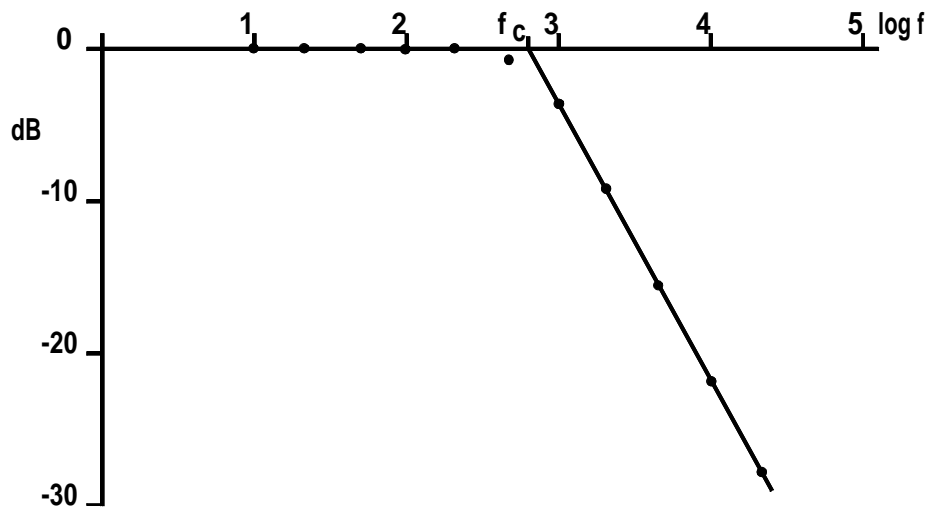

Corner frequency for first order filters


$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

For this example the corner frequency

$$f_c = \frac{1}{2\pi 2200 \times 0.1 \times 10^{-6}} = 724 \text{ Hz}$$

$\log(724) = 2.86$  and is marked as  $f_c$ .

---

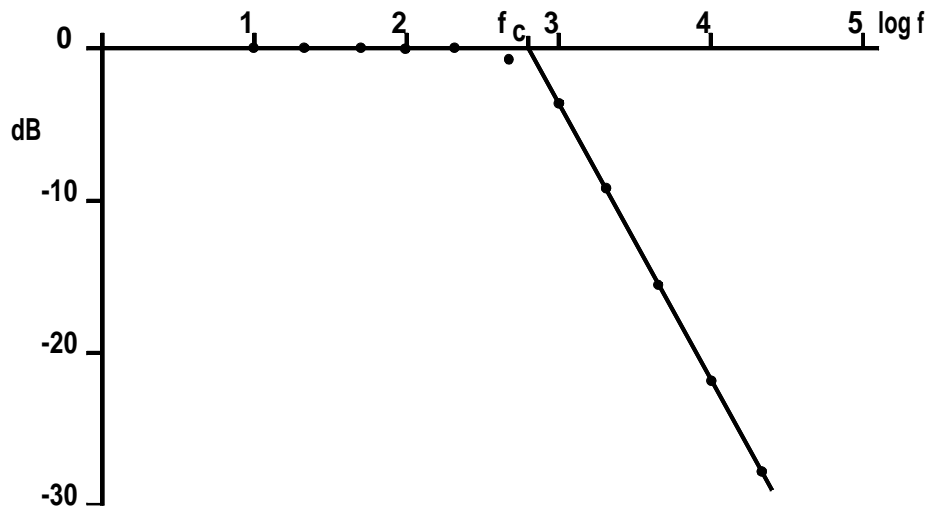

The response curve can be approximated by two straight lines through  $(\log f_c, 0\text{dB})$ .

One of the lines is at a constant 0dB and is the frequency axis.

The second line has a slope of -20 dB for each decade in frequency or each change of 1.0 on the log frequency scale.

Only need one number, the corner frequency, is needed to give a plot of the frequency response of an RC or RL circuit.


---

At the corner frequency  $\tan \phi = 2\pi f_c CR = 1$   
and therefore the attenuation is:-


$$\frac{1}{\sqrt{1 + \tan^2 \phi}} = \frac{1}{\sqrt{1 + 1}} = \frac{1}{\sqrt{2}} = .707$$

Expressed in dB this becomes  $20 \log 0.707 = -3 \text{ dB}$

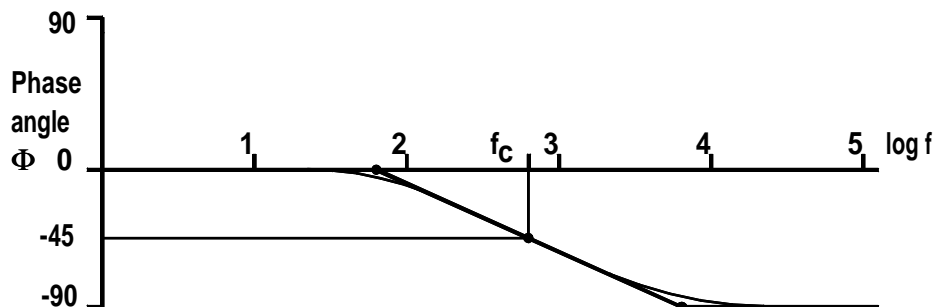so a small rounding off of the sharp corner made by the straight lines at the intersection accommodates this  $-3\text{dB}$  error at the corner frequency.



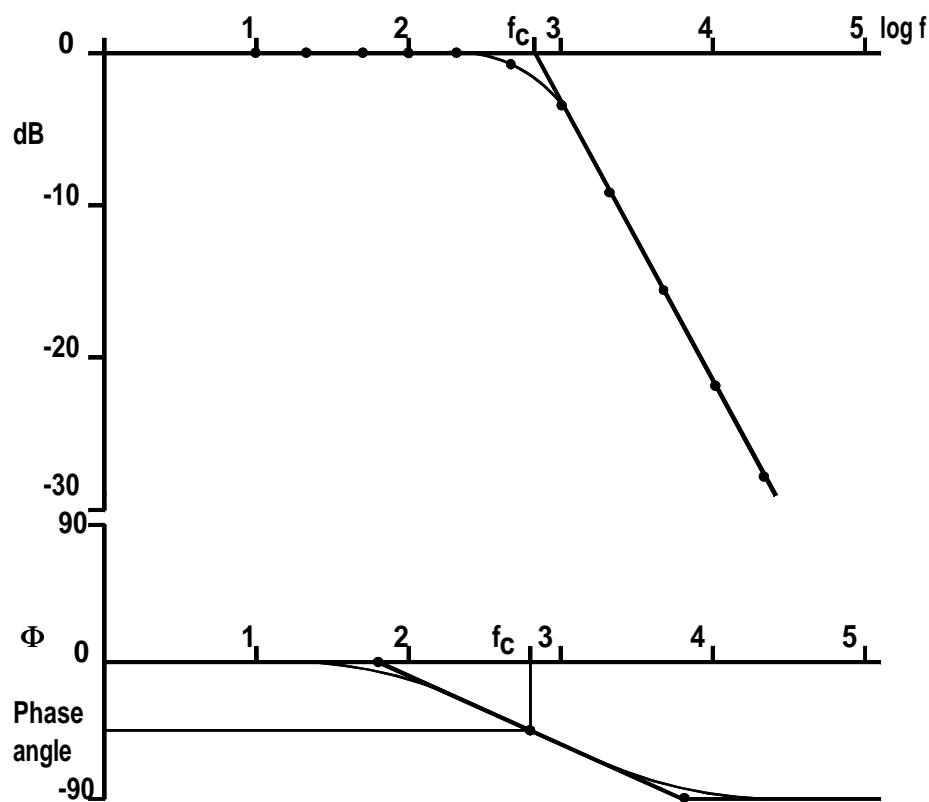When the amplitude response and the phase response are combined on one diagram with the log frequency scale the pair of curves is called a Bode Plot.



The RC circuit is a low pass circuit.

A CR circuit where the capacitor and resistor are interchanged is a high pass circuit.

When you have an RC circuit or a CR circuit the type of response can be easily determined by remembering that at low frequencies a capacitor is essentially an open circuit and at high frequencies a capacitor is a short circuit.

