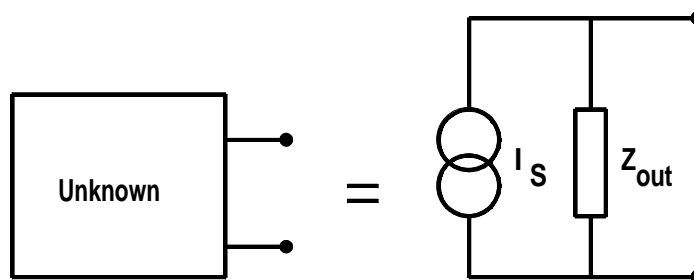


Any linear two terminal electronic system can be fully modelled by a current source,  $I_S$ , in parallel with a shunt impedance  $Z_{out}$ .


A current source drives a constant current through any circuit connected to it.

The circuit symbol used for a current source is two intersecting circles as shown in the diagram.



Norton's Theorem complements Thévenin's Theorem

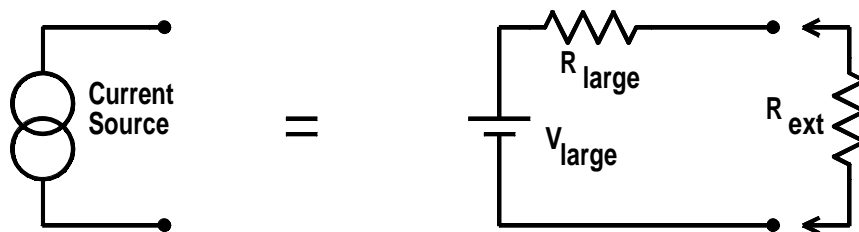Visualise a current source as a high voltage source in series with a large series resistor




For a wide range of externally connected resistors, the current will be essentially independent of the external resistance because if

$$R_{Large} \gg R_{ext}$$

$$\frac{V_{Large}}{R_{Large} + R_{ext}} \approx \frac{V_{Large}}{R_{Large}} = I_S$$

---

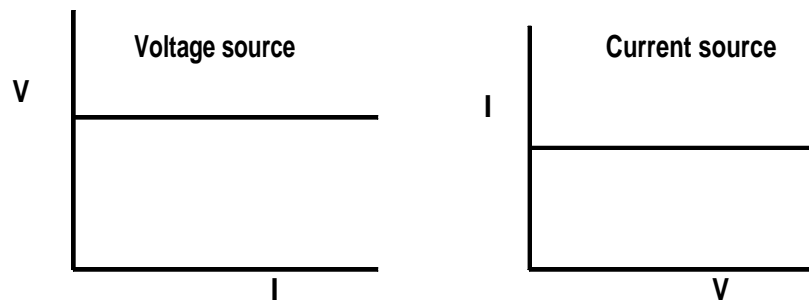

The characteristic curves for a voltage source and for a current source


---

In modelling circuit devices and systems, either the Thévenin or the Norton model can be used

Examples of devices and systems where the Thévenin approach is appropriate are:— batteries, diodes, DC constant voltage power supplies, audio and RF signal generators, lead acid battery chargers.

Examples of suitable applications of the Norton analysis approach are:— photo diodes in reverse bias, output characteristics of transistors and FETs in amplifiers, NiCd battery chargers, constant current supplies for fluorescent lamps and laboratory spectral lamps


---

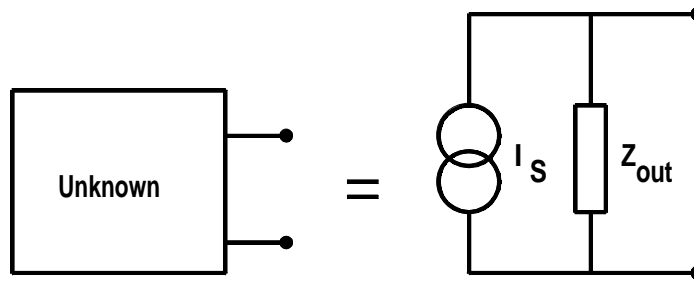

In order to measure the Norton equivalent of any circuit, it is only necessary to measure the open circuit voltage and the short circuit current.

- The current source is then given by:—  
 $I_S = \text{Short circuit current.}$

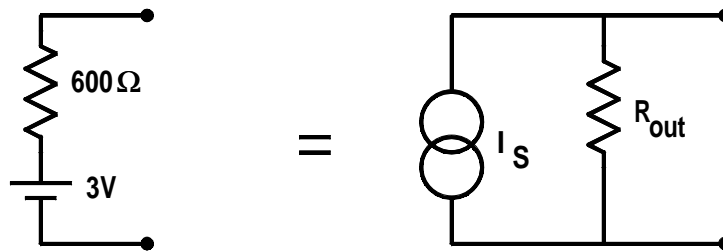- The output impedance is given by:—  
$$Z_{out} = \frac{V_{\text{open circuit}}}{I_{\text{short circuit}}}$$
-



Calculate the Norton equivalent circuit  
Short circuit current.

$$I_S = I_{\text{short circuit}} = \frac{V_{out}}{R_{out}}$$
$$= \frac{3V}{600\Omega} = 5mA$$


Open circuit voltage.

$$V_{out} = V_{\text{open circuit}} = I_S \times R_{out}$$

$$\text{therefore } 3V = 5mA \times R_{out}$$

$$R_{out} = \frac{3V}{5mA} = 600\Omega$$

---

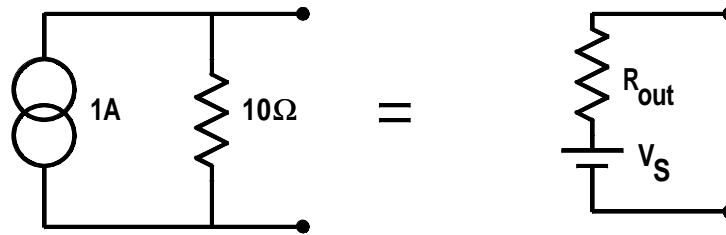

Convert from Norton to Thévenin equivalent circuit:— Calculate the Thévenin equivalent of the Norton circuit

Open circuit voltage.

$$V_{out} = I_S \times R_S = 1A \times 10\Omega = 10V$$

Short circuit.

$$I_{\text{short circuit}} = \frac{V_S}{R_{out}} = 1A$$

$$\text{Therefore } R_{out} = \frac{10V}{1A} = 10\Omega$$

---