
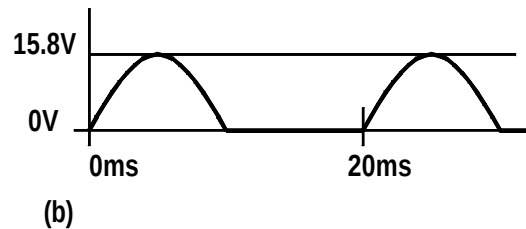


- A single diode, used as a rectifier, gives half wave rectification.
 - Four diodes in a bridge rectifier give full wave rectification.
 - Ripple voltage from a smoothed full wave rectifier $= \frac{I}{2 \times f \times C}$
-

Output voltage from half wave rectifier?

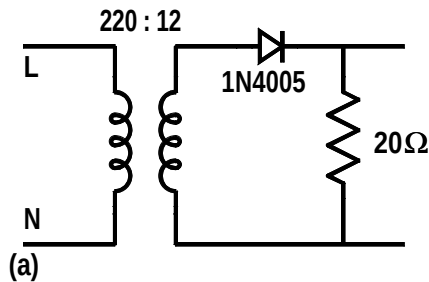





Output across load resistor $R_L = 20\Omega$
 Positive half cycles of the transformer output
 Minus the voltage drop across the diode.

$$V_{PEAK} = 1.4 \times V_{RMS} = 1.4 \times 12V = 16.8V$$

$$16.8V = 0.7V + 0.4 \times I + 20 \times I$$

$$\text{which gives } I = \frac{16.8 - 0.7}{20.4} = 0.79A$$
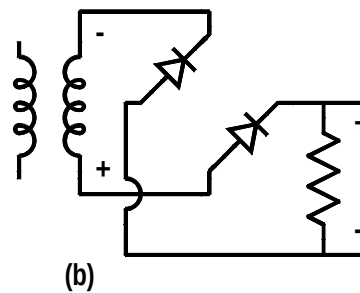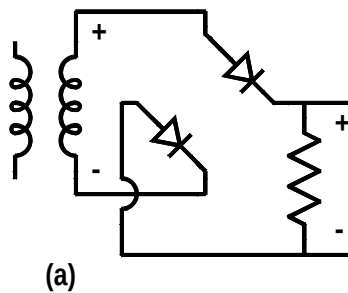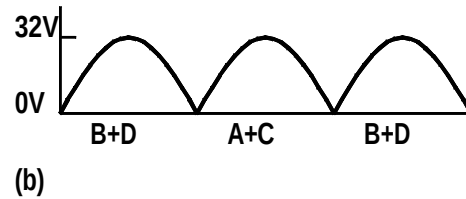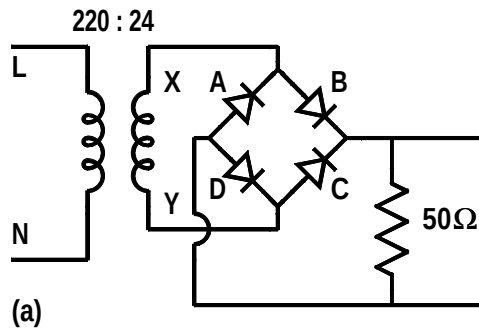
$$V_{out \max} = 20 \times 0.79 = 15.8V$$



Bridge rectifier output?

Two effective circuits for two half cycles.

$$V_{peak} = 24 \times 1.4 = 2 \times .7 + 2 \times I \times R_B + I \times 50\Omega$$

$$\text{If } R_B = 0.4\Omega, I_{peak} = 0.63A$$

$$V_{out\ peak} = 31.7V \quad \text{across the } 50\Omega$$


Advantage of the full wave rectifier

Less smoothing is required to convert the output to a DC.

Smaller transformer required

Less weight

Lower cost

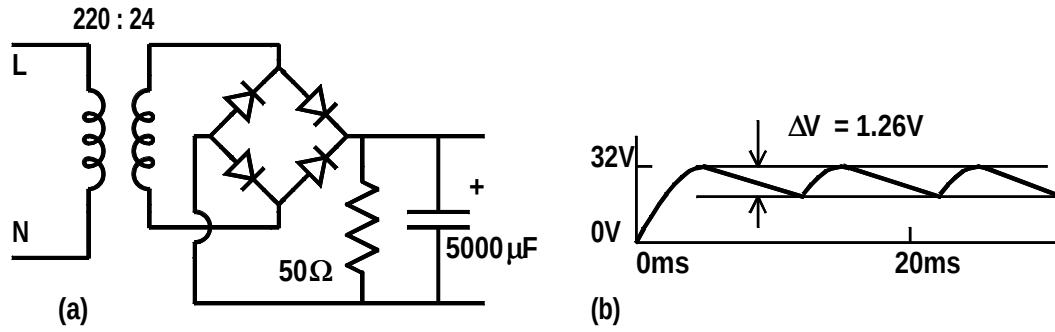

$$I_{out} = \frac{V_{out}}{R_L}$$

Charge out of the capacitor

$$\Delta Q = I_{out} \times \text{time} = \frac{I_{out}}{2 \times f}$$

$$\Delta Q = C \times \Delta V$$

Gives a ripple voltage

$$\Delta V = \frac{\Delta Q}{C} = \frac{I_{out}}{2 \times f \times C}$$

$$I_{out} = \frac{31.7\text{V}}{50\Omega} = 0.63\text{A}$$

$$\Delta V = \frac{I_{out}}{2 \times f \times C} = \frac{0.63}{2 \times 50 \times 5 \times 10^{-3}} = 1.26\text{V}$$

