

Two types of transistors:— npn and pnp.

A transistor is correctly biased when:—


- The emitter–base junction is forward biased.
- The base–collector junction is reverse biased.

The current gain $= \beta = h_{fe} = \frac{I_C}{I_B}$

Which gives $I_C = \beta \times I_B$

Typical values for β from 30 to 500.


$I_C \approx I_E$.

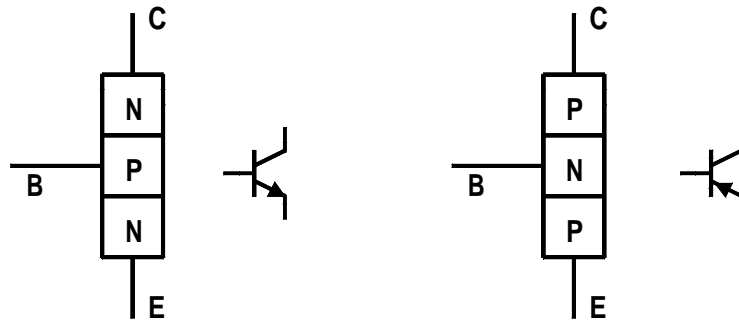

Bipolar transistor schematic structure

A transistor is a three layer device either an npn or a pnp structure.

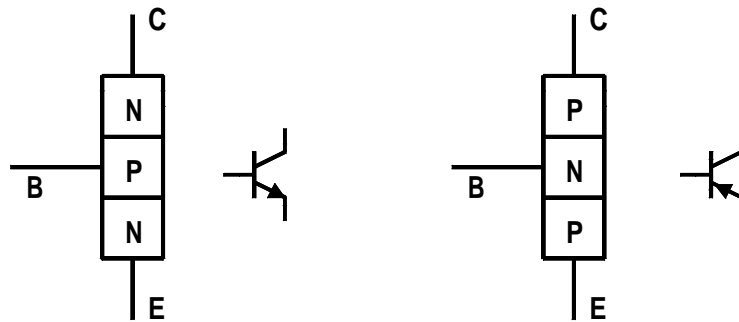Layers called emitter, base and collector



Bipolar transistor schematic structure


Emitter more heavily doped than base or collector

Three layers — two pn junctions

Junctions determine operation of transistor

For correct bias Voltages are applied so that emitter–base junction forward biased

base–collector junction reversed biased

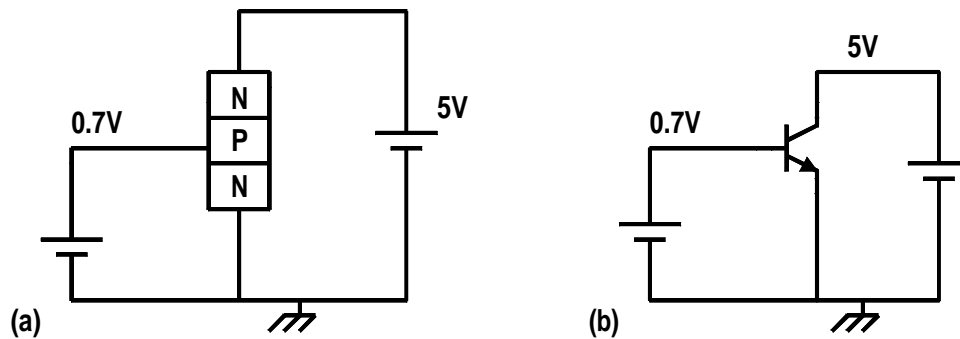


Correct biasing of npn transistor

Reverse biased pn junction is reversed biased for majority carriers only

The reverse current is due to flow of minority carriers across the junction

Reverse current is small because there are few minority carriers present

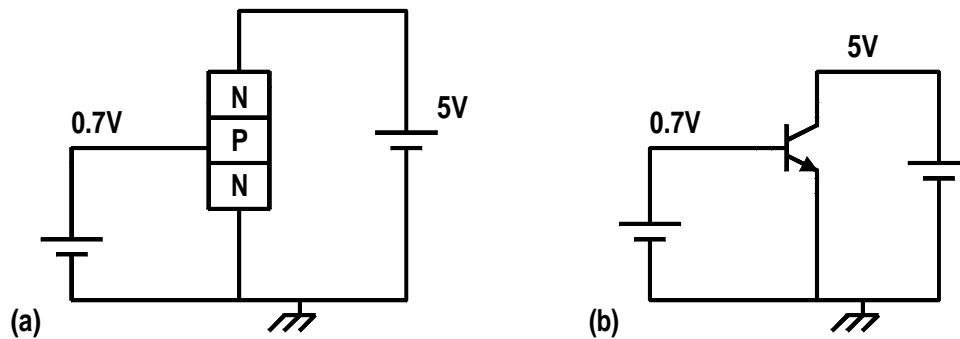Collector current should be small since the base–collector junction is reverse biased



Correct biasing of npn transistor

Forward biased emitter–base diode


n type doping of the emitter region is heavier than the p type doping of the base region

Current across the emitter–base junction mostly due to electrons flowing into the base region

Electrons diffuse until they reach the base–collector junction

At the base–collector junction electrons are swept across the junction to give a collector current

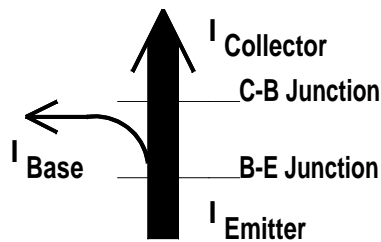Typically the base region is 0.2 microns thick.



Current is proportional to line thickness


$$I_C \approx I_E$$

A fraction of electrons injected into base from emitter recombine with p type holes in the base


Charging up of the base region to give an emitter–base junction which is no longer forward biased

A base current compensates for this

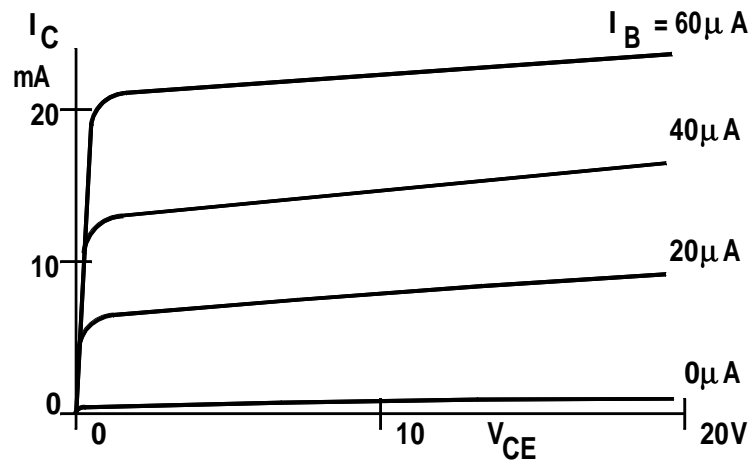Base current controls the larger emitter current and gives transistor its amplification properties.




BC109 Transistor output characteristic

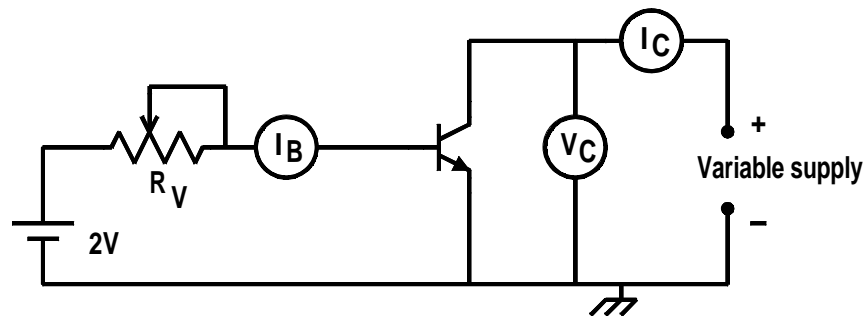

Circuit for measuring output characteristic

Two very important results

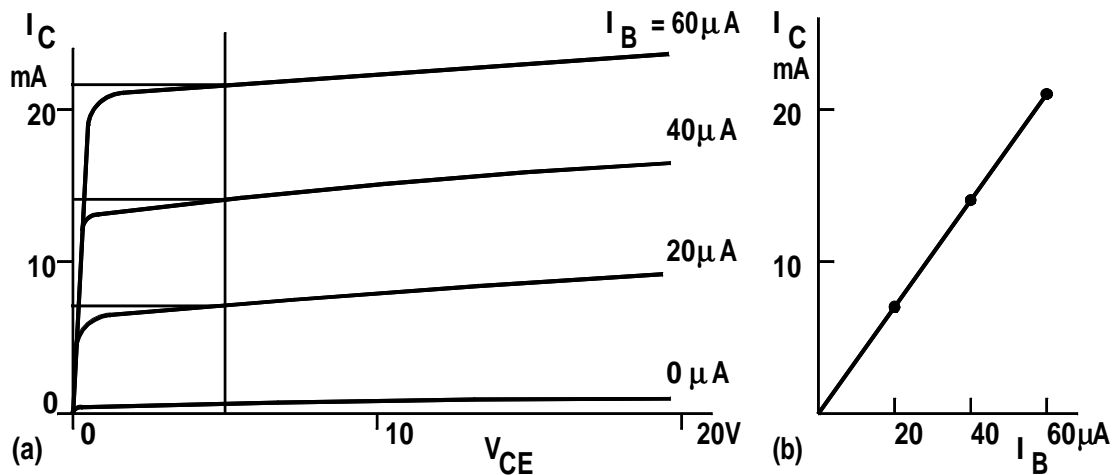- The collector current is relatively independent of the collector voltage.
 - The collector current is $\beta \times I_B$ where β is the current gain for the transistor. In some data sheets the value of β is quoted as h_{fe} where h_{fe} is used in the h parameter matrix method of transistor specification.
-



Calculate the current gain at $V_{CE} = 5V$

Draw a vertical line at 5V

Note the collector current, I_C

for $I_B = 0\mu A$, $20\mu A$, $40\mu A$, and $60\mu A$.

Plot these values for I_C as a function of I_B

$$\beta = \frac{dI_C}{dI_B} \approx \frac{20mA}{55\mu A} = 363$$

Unit 30 Transistor structure and operation

