

The function of a transistor bias circuit is to maintain

- a forward bias on the emitter–base junction
  - a reverse bias on the base–collector junction.
-

In transistor bias circuits  
Currents and voltages can  
usually be determined by using:—

$$\begin{aligned}I_C &= \beta \times I_B \\I_C &\approx I_E \\V_{BE} &\approx 0.7\end{aligned}$$

The basic equation for calculating the currents in transistor bias circuits is determined along a path such that:—



Voltage supply = Sum of voltage drops

---

A transistor must be biased so that  
the emitter–base junction is forward biased  
the base–collector junction is reverse biased.


Only a small number of circuits used to bias  
transistors and place the transistor in the  
middle of its operating range.

---

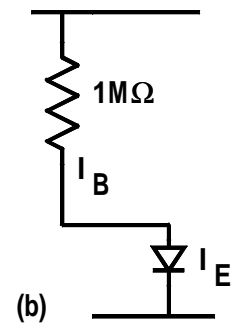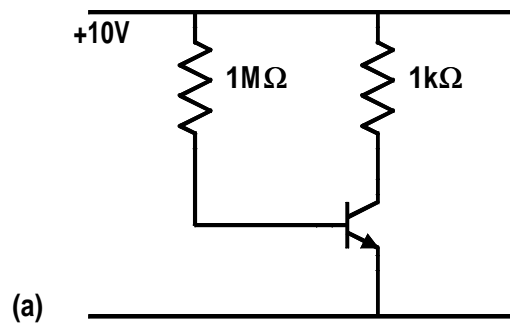

Calculate the emitter, base and collector voltages and currents for this circuit.  $\beta = 250$ .

---

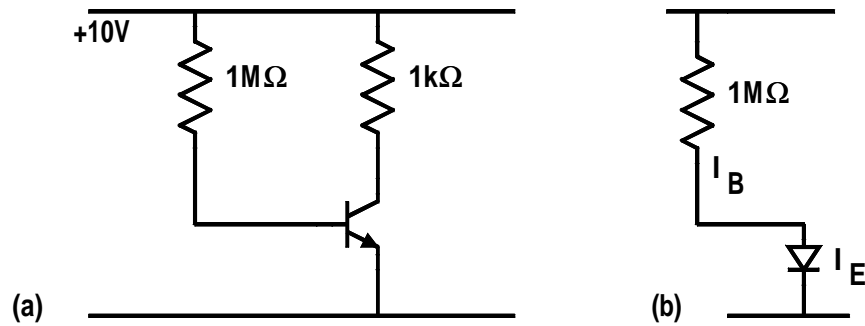

$$V_E = 0 \quad V_B = 0.7$$

Basic equation  $10V = I_B \times R_B + 0.7$

which gives  $10V = I_B \times 10^6 + 0.7$

and then  $I_B = \frac{10 - 0.7}{10^6} = 9.3\mu A$


$$I_C = \beta \times I_B = 250 \times 9.3\mu A$$

$$= 2.3mA$$

This gives  $V_C = 10 - I_C \times R_C$


$$= 10 - 2.3mA \times 1k\Omega$$

$$= 7.7V$$

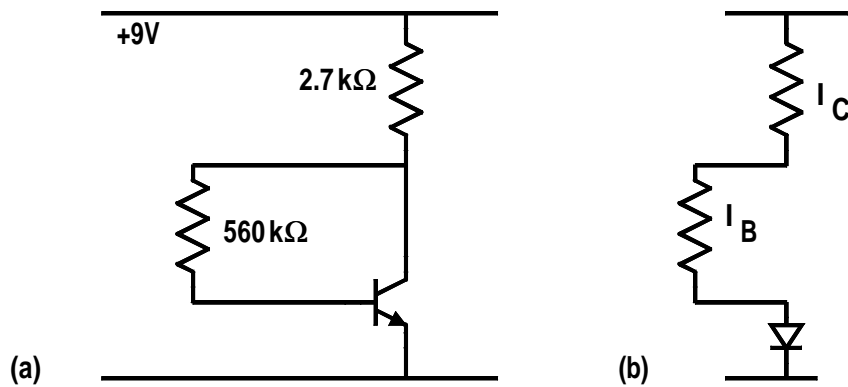

Calculate the emitter, base and collector voltages and currents for the circuit.  $\beta = 300$ .

---

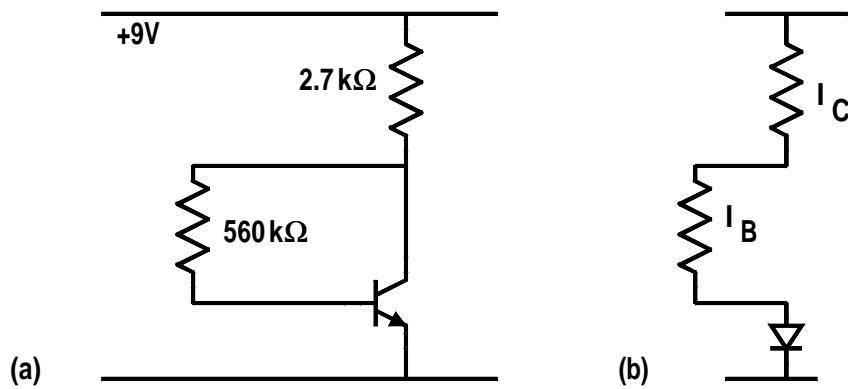

$$V_E = 0 \quad \text{and} \quad V_B = 0.7$$

$$\text{(B.E.) } 9V = I_C \times R_C + I_B \times R_B + 0.7$$


$$\text{Use } I_C = \beta \times I_B$$

$$\text{to get } 9 = \beta \times I_B \times R_C + I_B \times R_B + 0.7$$

$$\begin{aligned} \text{Solve } I_B &= \frac{9 - 0.7}{\beta \times R_C + R_B} \\ &= \frac{8.3}{300 \times 2.7 \times 10^3 + 560 \times 10^3} \\ &= 6.06 \mu A \end{aligned}$$

$$\text{Then } I_C = \beta \times I_B = 1.82 \text{ mA}$$

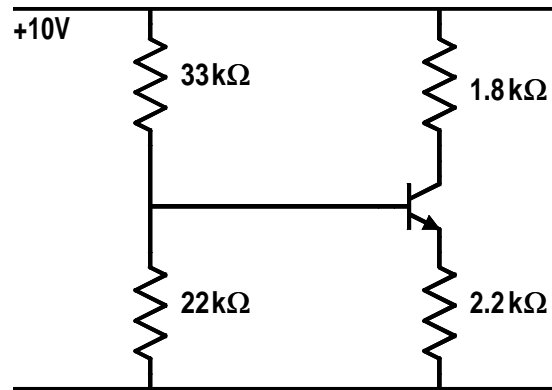
$$\begin{aligned} V_C &= 9V - 1.82 \text{ mA} \times 2.7 \text{ k}\Omega \\ &= 9 - 4.91 = 4.09V \end{aligned}$$



Calculate the emitter, base and collector voltages and currents for this circuit

---



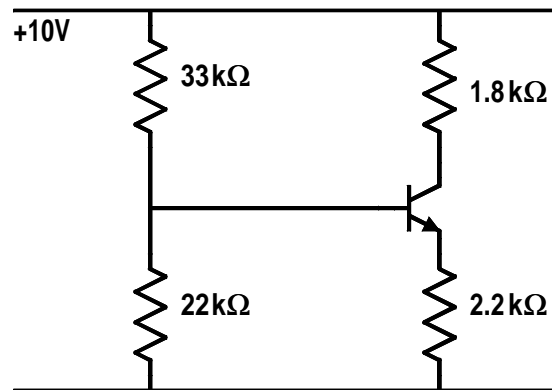


Basic equation along a path through the potential divider

Current into base is less than 10% of divider current.

$$\text{Potential divider current} = \frac{10V}{33k\Omega + 22k\Omega} = 182\mu A$$

$$\text{Then } V_B = \frac{22}{33 + 22} \times 10V = 180\mu A \times 22k\Omega = 4V$$

---

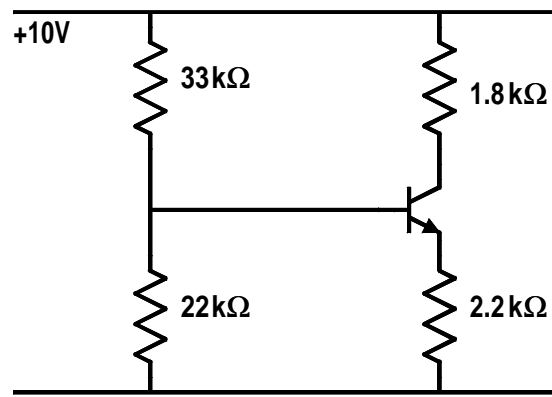

The base-emitter voltage is 0.7V and therefore:—

$$\begin{aligned}V_E &= V_B - 0.7 = 4.0 - 0.7 = 3.3V \\ \text{Then } I_E &= \frac{3.3V}{2.2k\Omega} = 1.5mA \\ I_C &= 1.5mA \\ V_C &= 10V - 1.8k\Omega \times 1.5mA \\ &= 10 - 2.7 = 7.3V\end{aligned}$$

Current gain  $\beta$  not used.

Good designs accomodates component tolerances.

$\beta$  varies from batch to batch

---