

JFET autobias	$R_S = \frac{V_{GS(off)}}{I_{DSS}}$
Gate source voltage	$V_{GS} \approx 0.4 \times V_{GS(off)}$
Drain current	$I_D \approx 0.4 \times I_{DSS}$
Common source gain	$A_V = -g_m \times R_D$

Typical gains about 10.

Typical input impedances about  $1M\Omega$ .


---

Only readily available parameters for a JFET such as the 2N3819, are  $I_{DSS}$ ,  $V_{GS(off)}$  and  $g_m$

Characteristic curves may be available from the component manufacturer but with delays.

Average values for that JFET type number  
Need a quick method of measuring the parameters for a particular JFET before using it.

---

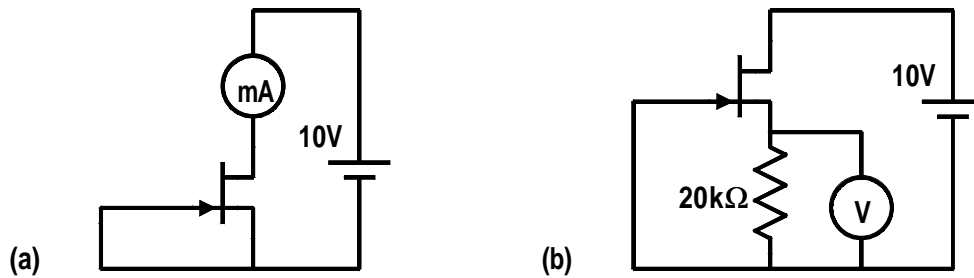

Circuits to measure  $I_{DSS}$  and  $V_{GS(off)}$  for a JFET

- (a) shows how the  $I_{DSS}$  can be measured directly
  - (b) gives Gate-Source cut off voltage  $V_{GS(off)}$
-

The equation for JFET drain current at any gate to source voltage is:–

$$I_D = I_{DSS} \times \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$$


Differentiate this to get:–

$$g_m = \frac{dI_D}{dV_{GS}} = -2 \frac{I_{DSS}}{V_{GS(off)}} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)$$

$g_m$  is called mutual conductance

Note that  $g_m$  is positive since both  $V_{GS}$  and  $V_{GS(off)}$  are negative quantities.

---

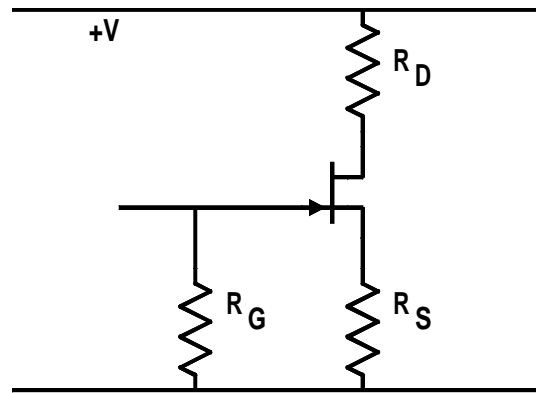


### JFET amplifier autobias circuit

Source current through the JFET also flows through  $R_S$  to give a reverse bias of  $I_D \times R_S$  between the gate and source.

The gate voltage is 0V because no significant current flows through  $R_G$  and through the reverse biased gate to channel junction.

---

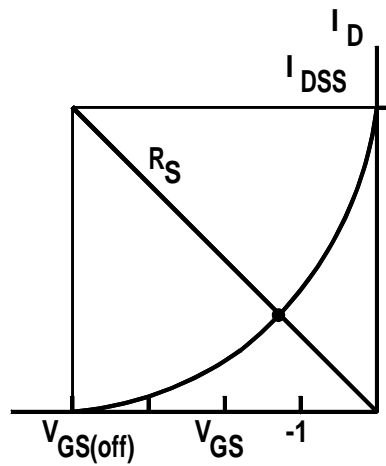

Method of selecting  $R_S$

Wide range of possible values for  $R_S$

$$\text{Use } R_S = \frac{V_{GS(off)}}{I_{DSS}}$$

Causes the bias point to be at the intersection of the line for  $R_S$  and the curve for  $V_{GS}$

---

$$V_{GS} = I_D \times R_S = I_D \times \frac{V_{GS(off)}}{I_{DSS}}$$

$$\text{which gives } \frac{V_{GS}}{V_{GS(off)}} = \frac{I_D}{I_{DSS}}$$

Put into equation for  $I_D$  for the JFET

$$\frac{I_D}{I_{DSS}} = \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$$

Gives an equation of the form  $x = (1 - x)^2$   
which has solutions  $x \approx 2.6$  and  $x \approx 0.4$ .

$$\text{Use } \frac{V_{GS}}{V_{GS(off)}} = \frac{I_D}{I_{DSS}} = 0.4$$

$$\text{and then } I_D = 0.4 \times I_{DSS}$$

---

Select value for drain resistance,  $R_D$ .

The mutual conductance,  $g_m$ , relates the change in drain current to a change in the gate voltage:—

$$g_m = \frac{dI_D}{dV_{GS}} = \frac{i_d}{v_g}$$

The drain resistor relates the change in drain current to the change in the output voltage:—


$$v_d = -R_D \times i_d$$

Combine to get small signal voltage gain:—

$$A_V = \frac{v_{out}}{V_{in}} = \frac{v_d}{v_g} = \frac{-R_D \times i_d}{\frac{i_d}{g_m}} = -g_m R_D$$

---



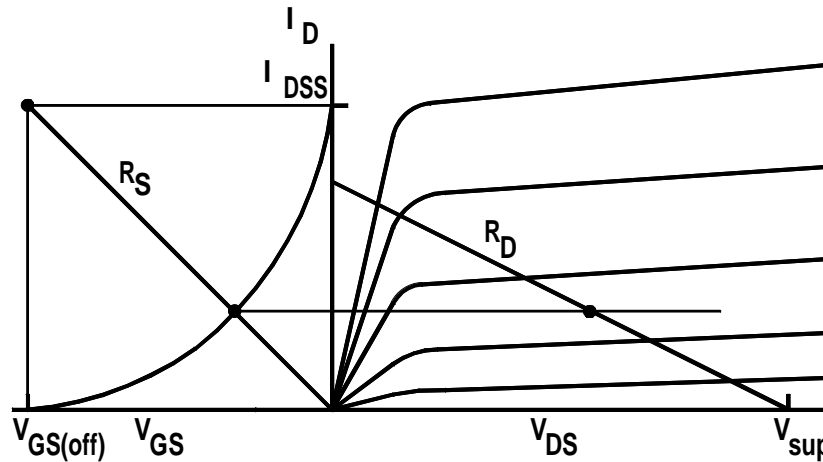

If  $A_V$ , is specified then

$$R_D = \frac{A_V}{g_m}$$

Draw load line

Load line of slope  $R_D$  drawn through  $2 \times 0.4 I_{DSS} = 0.8 I_{DSS}$  on the  $I_D$  axis

$$\text{Select } V_{sup} = 0.8 \times I_{DSS} \times R_D$$


$$g_m \approx 2000\mu S \text{ and } R_D \approx 5k\Omega$$

gains of the order of  $g_m \times R_D = 10$  are expected

Gains are much lower than values of 200 for bipolar transistor amplifiers.

Input impedance is high


---

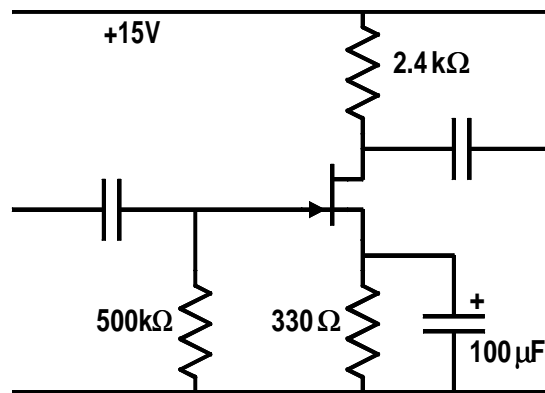

Calculate the component values and supply voltage to obtain a small signal voltage amplification,  $A_V = -6$  and an input impedance of  $500k\Omega$ .


$g_m = 2500\mu S$ ,  $V_{GS(off)} = 2.5V$  and  $I_{DSS} = 7.5mA$ .


---

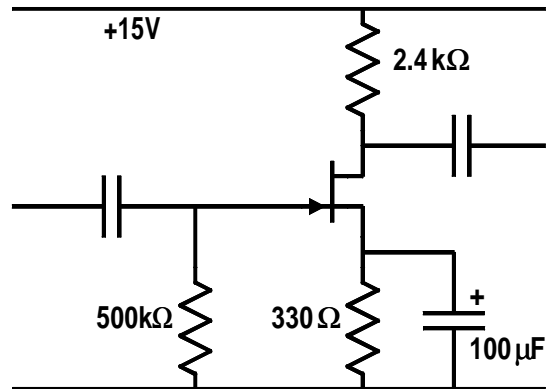

$R_G = 500k\Omega$  gives required input impedance
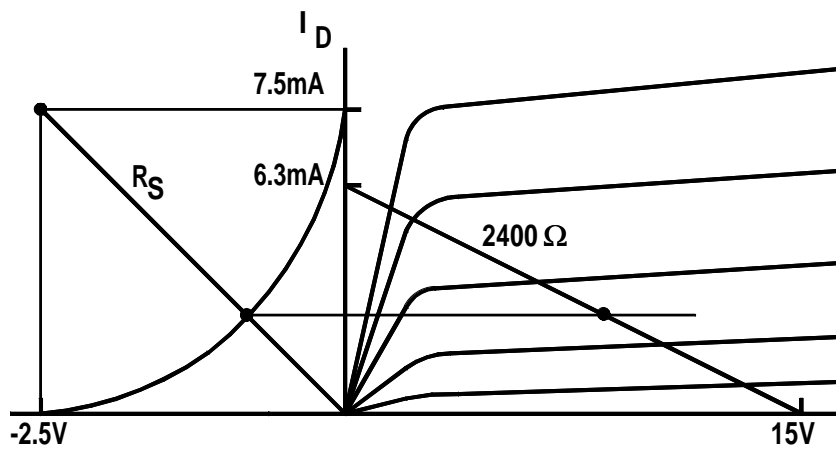
$$\text{Let } R_S = \frac{V_{GS(off)}}{I_{DSS}} = \frac{2.5V}{7.5mA} = 330\Omega$$



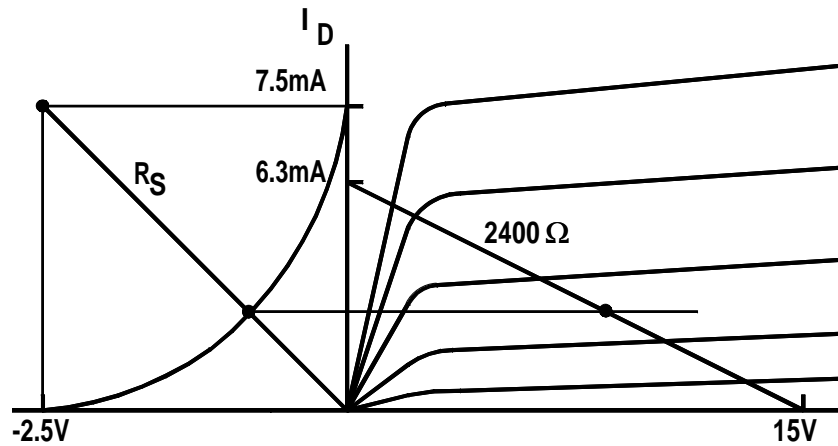

gain of -6 therefore

$$A_V = -6 = -g_m \times R_D = -2500 \times 10^{-6} \times R_D$$

$$\text{gives } R_D = \frac{6}{2500 \times 10^{-6}} = 2400\ \Omega = 2.4\text{k}\Omega$$

It can be seen that a supply voltage of 15V gives a reasonable intersection point.