

- Active filters contain active devices such as transistors or op-amps so as to give gain as well as filtering action.
 - The main advantage of active filters is that their performance can be made to be more independent of the signal source and load impedances.
 - An iterative process is usually used to choose the best of the many possible designs for a particular application.
-

Passive filters are simple.

Performance depends on source and load.

Active filters give more reliable performance.

Many designs for specific purposes.

We examine audio frequency filters which use op-amps.

Three filter types

- Low pass
- High pass
- Band pass



Use an iterative process for design.

A set of equations is given for each filter.

Many possible values for R and C

Avoid extreme values of R and C.

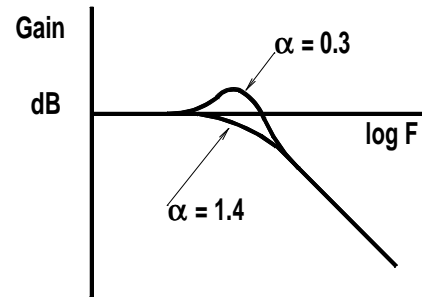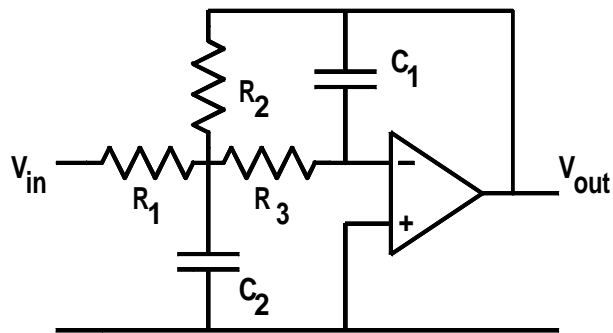Use values of R within the range 100Ω to $1M\Omega$ and values for C within the range $1nF$ to $1\mu F$.





Guess initial values for components and follow through the calculation to see if the other dependant components have reasonable values.

Repeat the calculations with a better guess.

Peaking factor, α , describes the sharpness of the edge of a low or high pass filter.

α	0.1	0.3	1.0	1.4
<i>dB</i> peaking	20	10	3	0
Gain increase	10	3.16	1.4	1.0

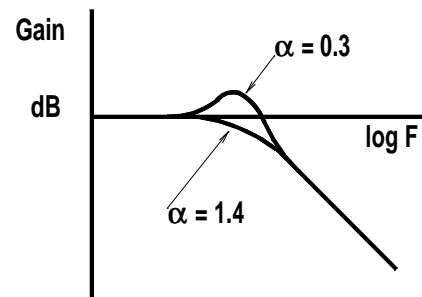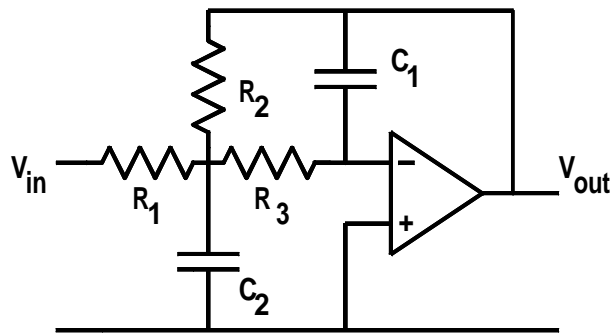

Low Pass Filter

Target design F = Cutoff frequency, Hz

α = Peaking factor

A = gain



Initial Estimate C_1 in μF

$$\text{Then } C_2 = \frac{4(1 + A)C_1}{\alpha^2} \mu F$$

$$R_2 = \frac{\alpha \times 10^6}{4\pi F C_1}$$

$$R_1 = \frac{R_2}{A}$$

$$R_3 = \frac{R_2}{1 + A}$$

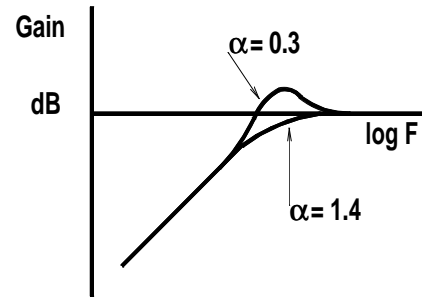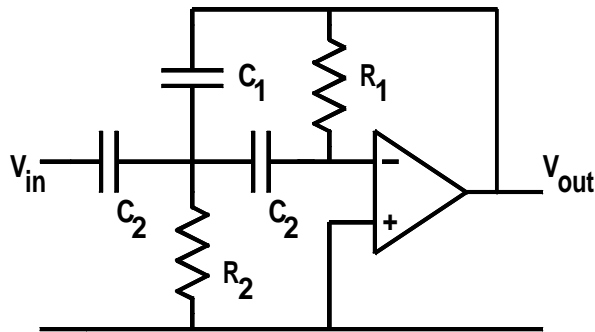

High Pass Filter

Target design F = cutoff frequency, Hz

α = peaking factor



A = gain

Initial estimate C_2 in μF

Then $C_1 = \frac{C_2}{A} \mu F$

$$R_1 = \frac{(2A + 1) \times 10^6}{2\pi F \alpha C_2}$$
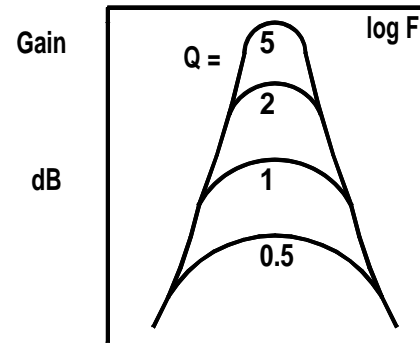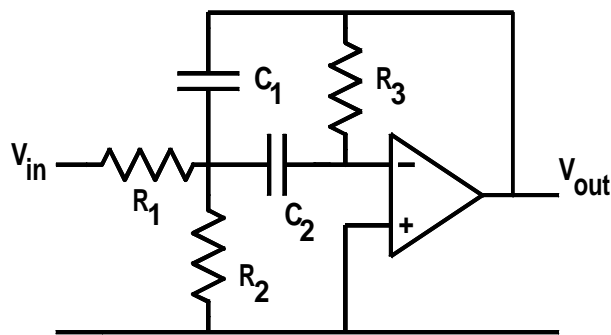
$$R_2 = \frac{\alpha A \times 10^6}{2\pi F C_2 (2A + 1)}$$



Band Pass Filter

Target design B = Bandwidth, Hz



Estimate C_1 C_2 in μF

$$\text{Then } Q = \frac{F}{B}$$

$$R_1 = \frac{Q \times 10^6}{2\pi F A C_1}$$



$$R_2 = \frac{1}{2\pi F Q (C_1 + C_2) \times 10^{-6} - \frac{1}{R_1}}$$
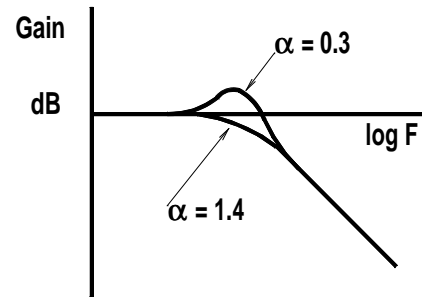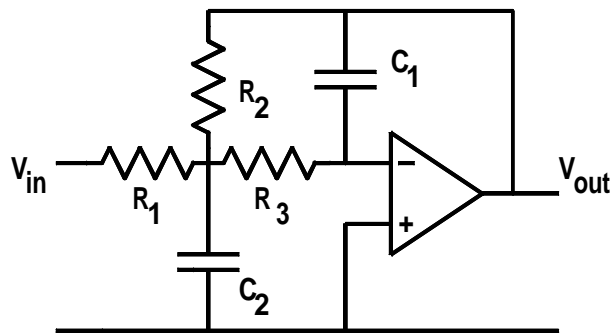
$$R_3 = \frac{Q \times 10^6}{2\pi F} \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$





Design a low pass filter for a cutoff frequency of 1500Hz , a gain of 12 and 3dB of peaking at the band edge.

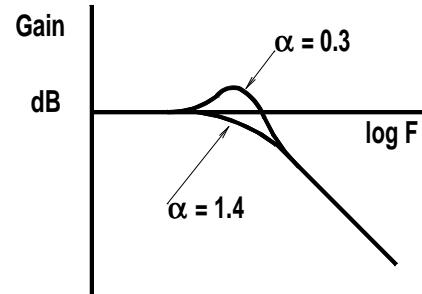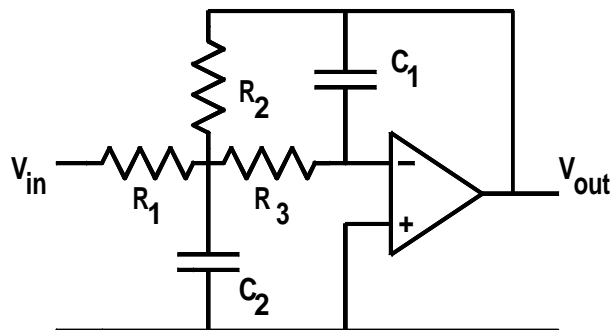Use the circuit of Figure 48.1. A peaking of 3dB at the band edge corresponds to a peaking factor of $\alpha = 1$, from the table.



Estimate C_1 and use the formulae for C_2 , R_1 , R_2 and R_3 .

It.	1	2	3	4	5	6	
C_1	1.0	.1	.01	.001	.0005	.0001	μF
C_2	52	5.2	.52	.052	.026	.005	μF
R_1	4.4	44	442	4.4k	8.8k	44k	Ω
R_2	53	530	5.3k	53k	106k	530 k	Ω
R_3	4.1	41	410	4.1k	8.2k	41k	Ω

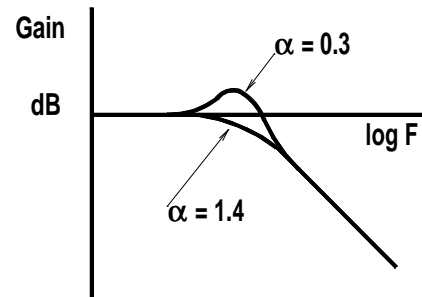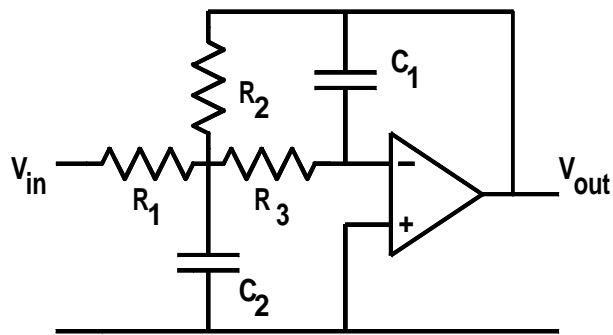


In principle, all of these calculations give valid and correct filter design values.

In practice, iterations 1, 2 and 3 have low resistances

Iteration 6 and any further iterations with smaller values of C_1 have over large values of R

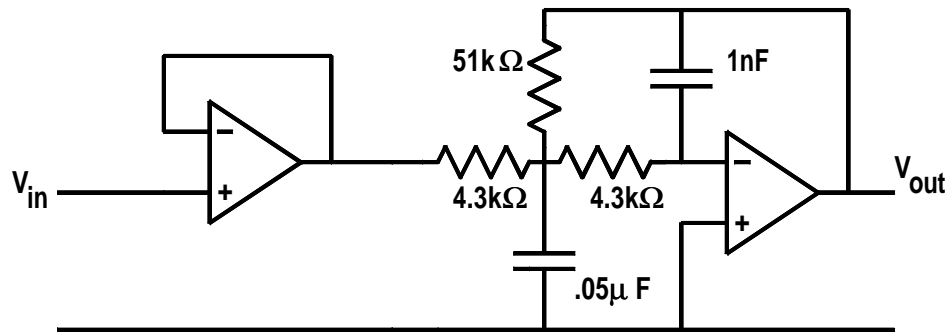In this example, iteration no 4 is a reasonable compromise.



We do not know the signal source resistance, so it is good practice to isolate the filter from the signal source by using a voltage follower stage in the input which has a high input impedance and low output impedance.
