

- Charging RC circuit

$$V_C = V_{sup} \left( 1 - e^{\frac{-t}{RC}} \right)$$

- Discharging RC circuit

$$V_C = V_{sup} e^{\frac{-t}{RC}}$$

- Charge up time or discharge time between  $\frac{1}{3}V_{sup}$  and  $\frac{2}{3}V_{sup}$  is

$$T = 0.7RC$$


- Time to charge from 0V to  $\frac{2}{3}V_{sup}$  is

$$T = 1.1RC$$

- Time intervals for a 555 Timer IC are

$$T_1 = 0.7(R_A + R_B)C \quad \text{and} \quad T_2 = 0.7R_B C$$

---

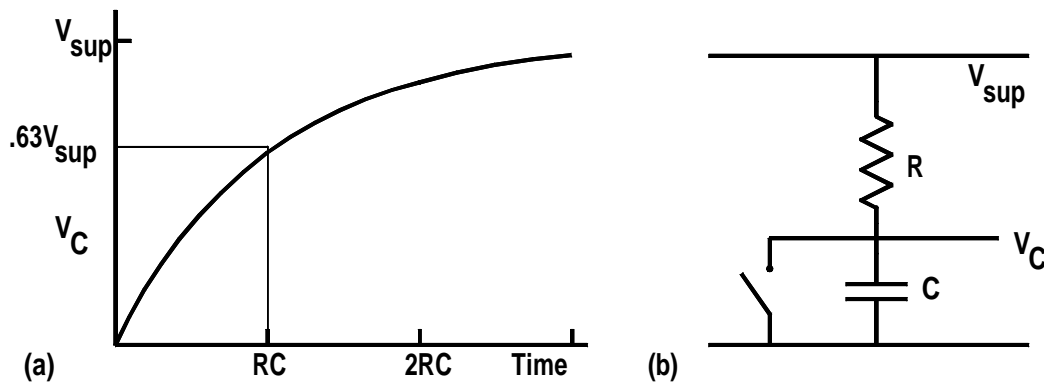

$RC$  charging curve.

$V_{sup} - V_C$  across  $R$ .

Then  $I = \frac{dQ}{dt} = \frac{V_{sup} - V_C}{R}$ . Charge on capacitor is  $Q = CV_C$


After differentiation becomes  $\frac{dQ}{dt} = C \frac{dV_C}{dt}$ . Equate these two expressions for the current to get

$$RC \frac{dV_C}{dt} = V_{sup} - V_C$$

Solution is

$$V_C = V_{sup} \left( 1 - e^{\frac{-t}{RC}} \right)$$

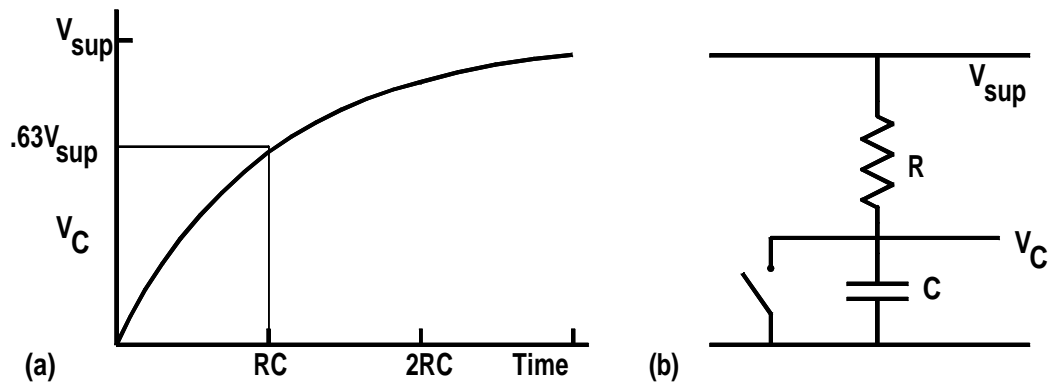where  $RC$  is called the time constant.



*RC* charging curve.

At the time  $T = RC$ , the calculated value of the  $V_C$  is  $0.63V_{sup}$ .


The output has made 63% of its total change at time  $T = RC$ .

This 63% response is used in instrumentation.

Thermometer time constants.

Wait 3 time constants for valid reading.

---

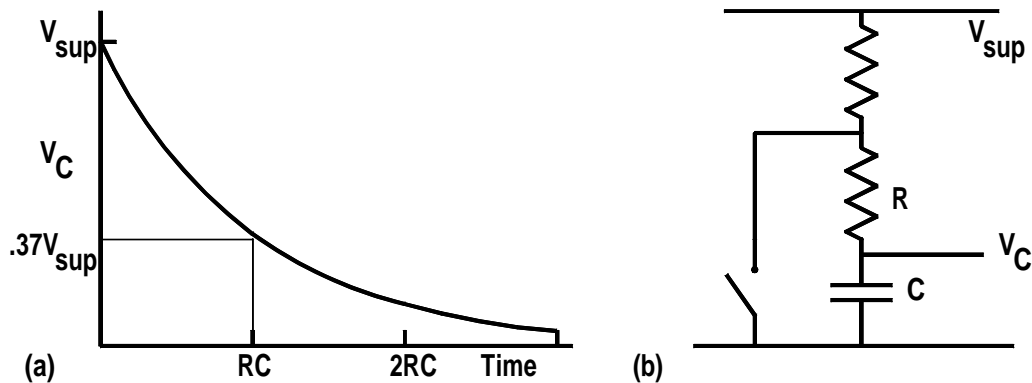

$RC$  discharging curve.

Close switch at  $t = 0$


Set up differential equation

$$V_C = V_{sup} e^{\frac{-t}{RC}}$$

Define  $T_L$  is time for capacitor to charge from  $0V$  to the lower voltage  $V_L$ .

Define  $T_H$  as time for capacitor to charge from  $0V$  to the higher voltage  $V_H$ .

---

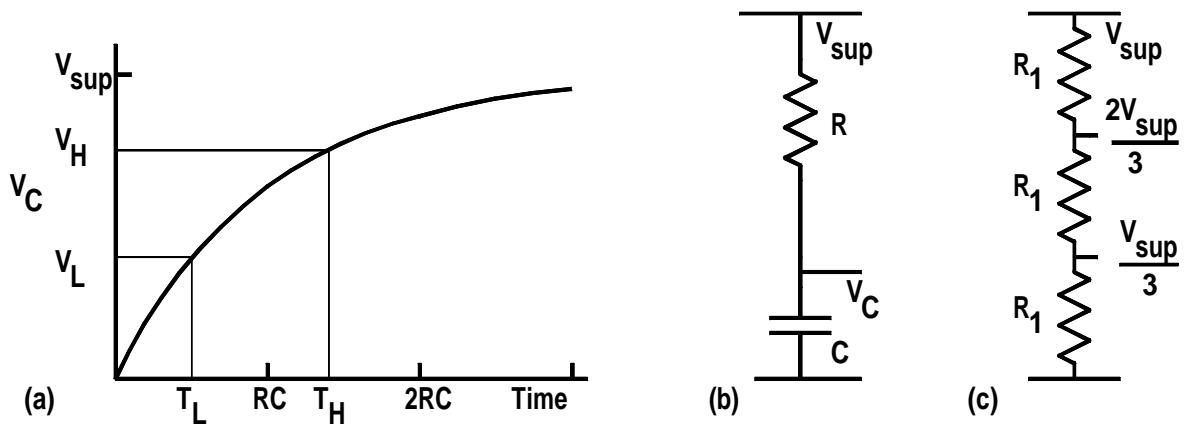

Time between voltages  $V_L$  and  $V_H$ .

$$V_L = V_{sup} \left( 1 - e^{\frac{-T_L}{RC}} \right)$$

and

$$V_H = V_{sup} \left( 1 - e^{\frac{-T_H}{RC}} \right)$$


Rearrange and take natural logs

$$-T_L = RC \ln \left( \frac{V_{sup} - V_L}{V_{sup}} \right)$$

and

$$-T_H = RC \ln \left( \frac{V_{sup} - V_H}{V_{sup}} \right)$$


---

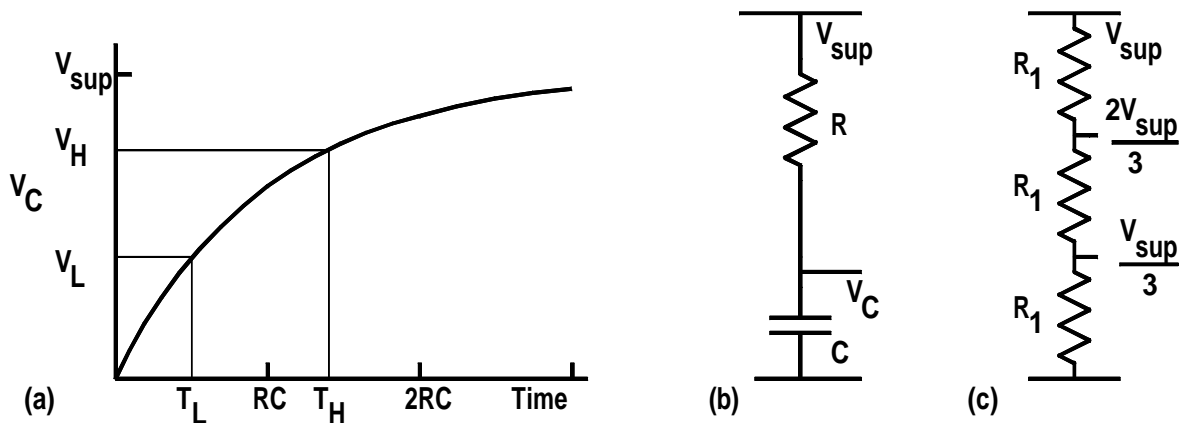


Subtract

$$\begin{aligned}
 T_H - T_L &= RC \left( \ln \left( \frac{V_{sup} - V_L}{V_{sup}} \right) - \ln \left( \frac{V_{sup} - V_H}{V_{sup}} \right) \right) \\
 &= RC \ln \left( \frac{V_{sup} - V_L}{V_{sup} - V_H} \right)
 \end{aligned}$$

Set  $V_L = \frac{1}{3}V_{sup}$  and  $V_H = \frac{2}{3}V_{sup}$ . Put into expression for  $T_H - T_L$

$$T = RC \ln \left( \frac{V_{sup} - \frac{1}{3}V_{sup}}{V_{sup} - \frac{2}{3}V_{sup}} \right) = RC \ln 2 = .693RC \approx 0.7RC$$



---

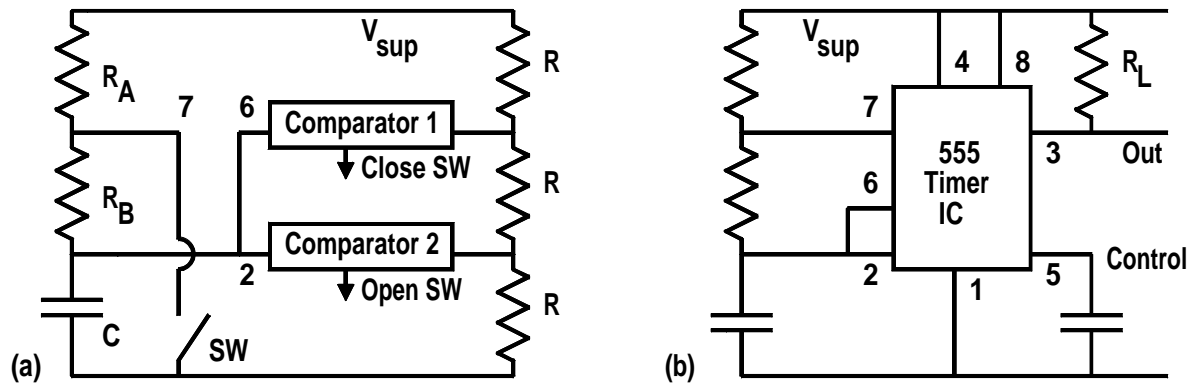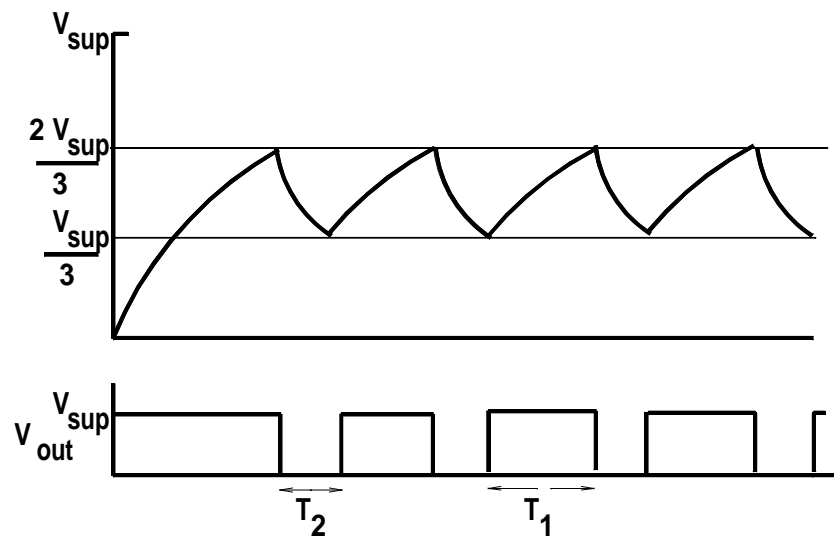

Internal circuit blocks of the 555 Timer.

Three resistors in series give reference voltages of  $\frac{1}{3}V_{sup}$  and  $\frac{2}{3}V_{sup}$ .

Comparators toggle a switch SW



Capacitor and output voltage waveforms for the 555 Timer.

Pin 3 gives an output signal which is an indicator of the state of the IC comparators.

Time  $T_1$  to charge from  $\frac{1}{3}V_{sup}$  to  $\frac{2}{3}V_{sup}$  is


$$T_1 = 0.7(R_A + R_B)C$$

Time to discharge from  $\frac{2}{3}V_{sup}$  to  $\frac{1}{3}V_{sup}$  is

$$T_2 = 0.7R_BC$$


---




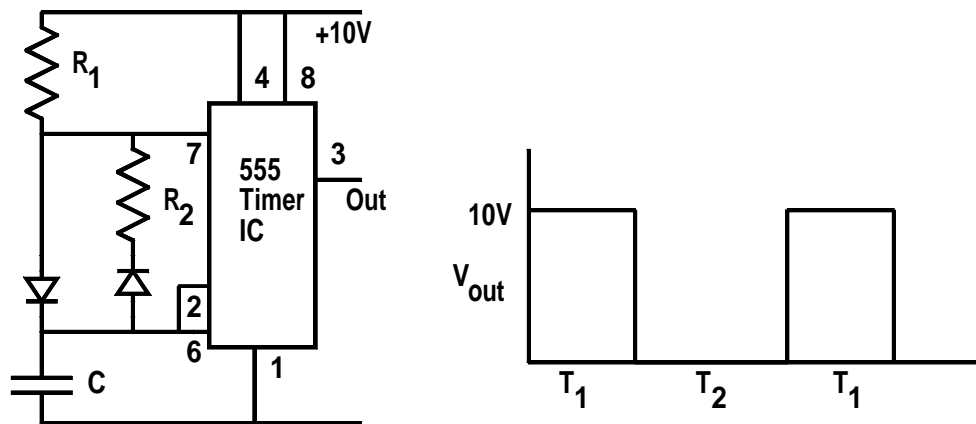


Circuit for generation of arbitrary Mark Space ratio.

Capacitor charges through  $R_1$  and the diode with a time constant of  $T_1 = 0.7R_1C$ .

The discharge path is through  $R_2$  and the diode in series with  $R_2$  to give a time constant  $T_2 = 0.7R_2C$ .


---

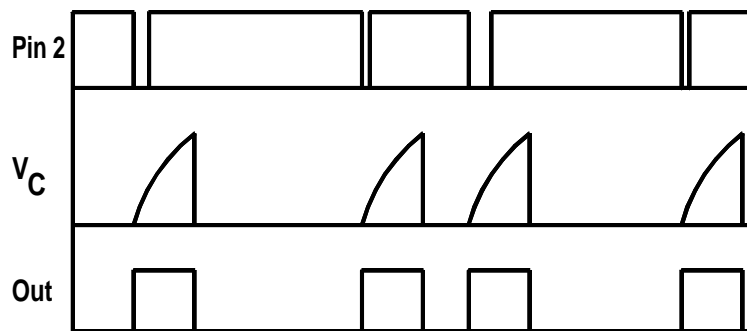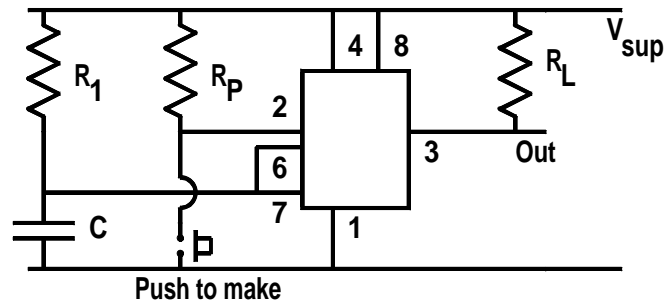

Triggered operation of the 555 Timer.

Monostable operation instead of astable operation.

---

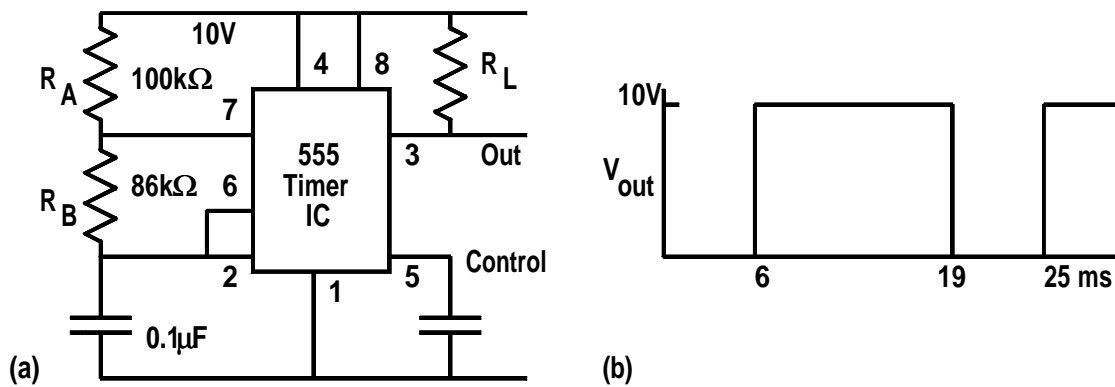

555 Timer circuit to give 0V for 6ms followed by 10V for 13ms.

Choose  $C = 0.1\mu F$ .

$$T_2 = 6 \times 10^{-3} = 0.7 \times .1 \times 10^{-6} \times R_B$$

and therefore  $R_B = \frac{6 \times 10^{-3}}{.7 \times .1 \times 10^{-6}} = 86k\Omega$

$$T_1 = 13 \times 10^{-3} = .7 \times .1 \times 10^{-6} (86k\Omega + R_A)$$

and therefore  $86k\Omega + R_A = 186k\Omega$  which gives

$$R_A = 100k\Omega$$