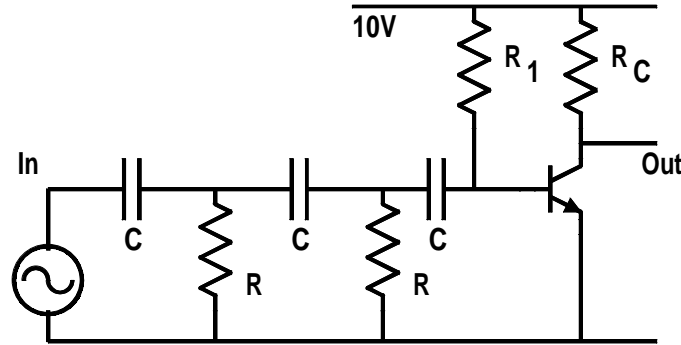


- Sinusoidal voltage waveforms are obtained by using an amplifier
    - In positive feedback,
    - A loop gain of 1 and
    - A frequency selective feedback network.
-




Phase shift network and amplifier. A sinusoidal signal applied to the input is phase shifted and attenuated in each of the three  $CR$  filters.

$$\phi_1 = \tan^{-1} \left( \frac{1}{2\pi fCR} \right)$$

Inversion corresponds to a phase shift of  $180^\circ$ .

$$\phi_{total} = 3\phi_1 + 180^\circ$$

---

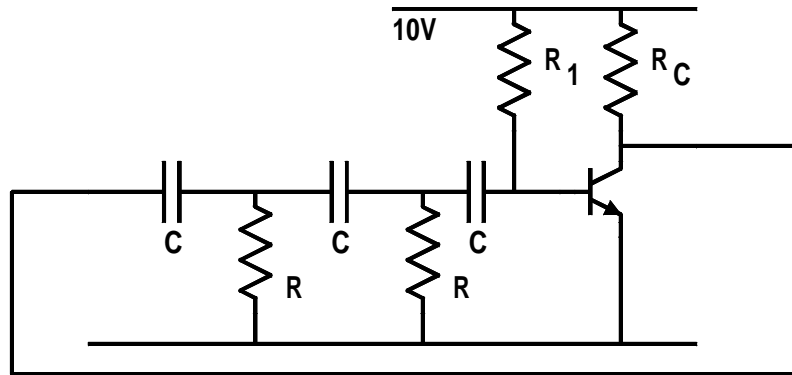


Phase shift oscillator.

Loop gain greater than 1

Oscillation at  $f_o = \frac{1}{2\sqrt{3}\pi CR}$


---

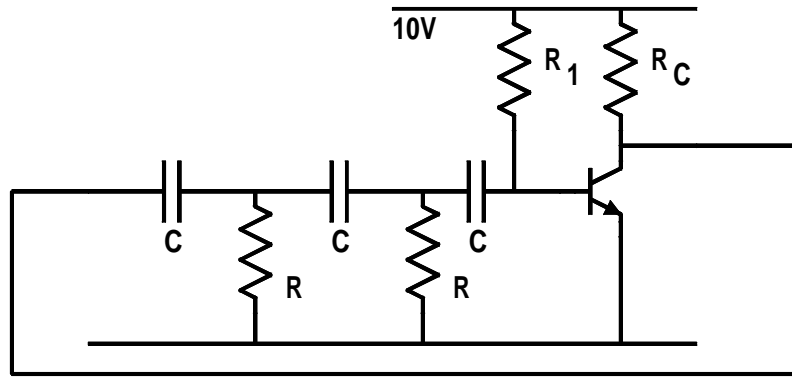

Positive feedback causes the circuit to go into oscillation.

Loop gain greater than 1  
Barkhausen Criterion.

---

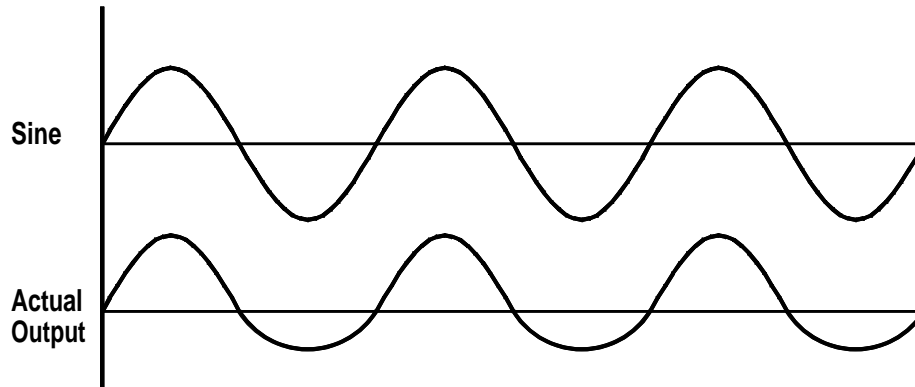


Distortion due to saturation nonlinearity.

Transistor amplifier ceases to be fully linear when large signals are present.

Reduce the gain to give a loop gain of 1.

This is called amplitude stabilization.

---

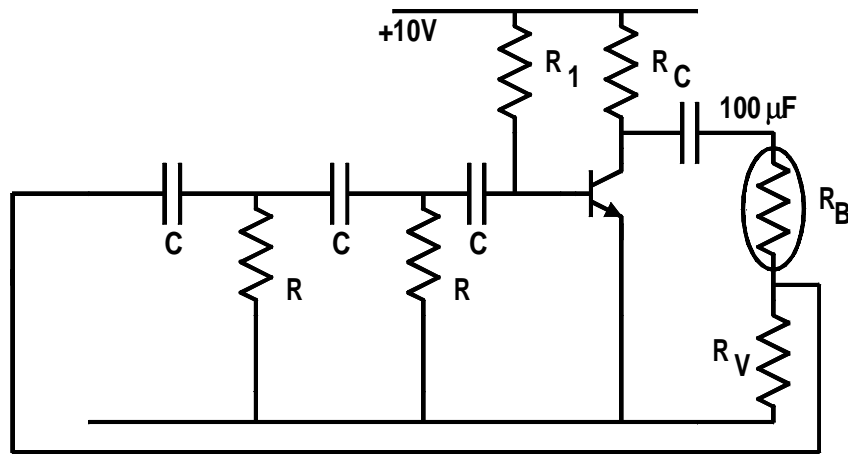


Amplitude stabilization by control of feedback.

Use a nonlinear device such as a bulb or thermistor.

Feedback fraction is changed.

---

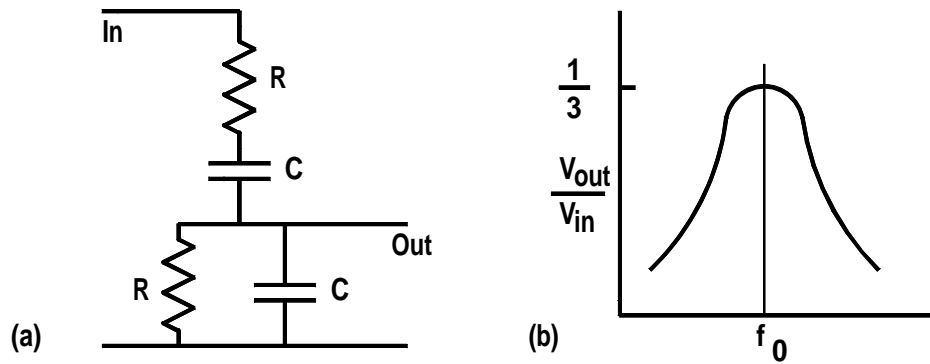


Wein bridge and response.

First consider a Wein bridge

This is a bandpass filter which has the response curve shown.

The frequency at the peak of the passband is  $f_o = \frac{1}{2\pi RC}$ .

---

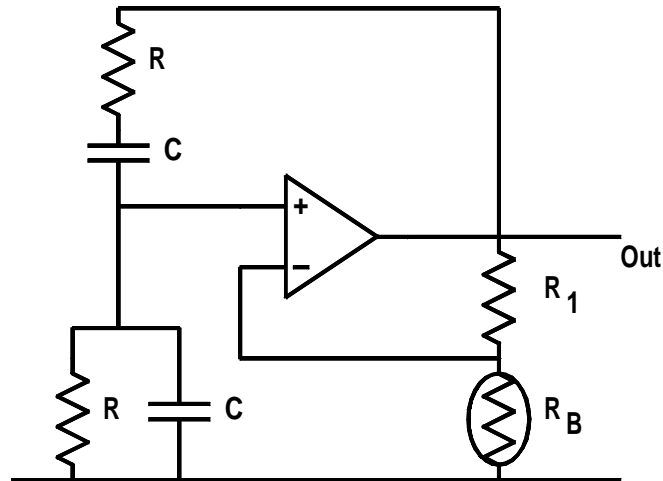


Wein bridge oscillator.

The attenuation at the peak of the Wein bridge response is  $\frac{1}{3}$

Gain of amplifier must be at least 3 for oscillation to take place


---



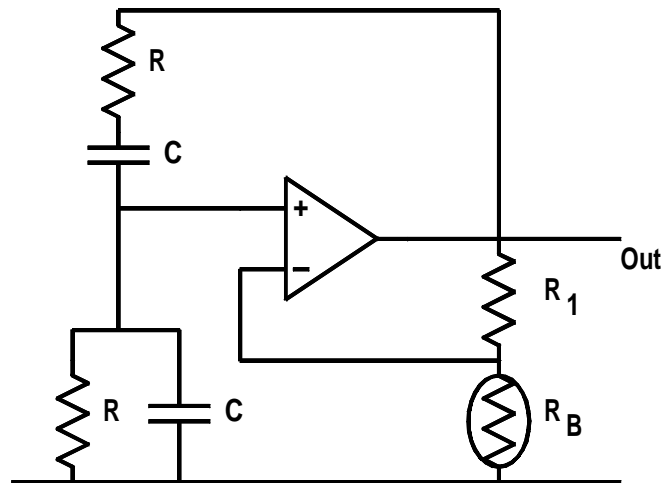

Frequency control with a twin ganged potentiometer for the two Wein bridge resistors. Decade changes of frequency are obtained by switching in pairs of capacitors

---

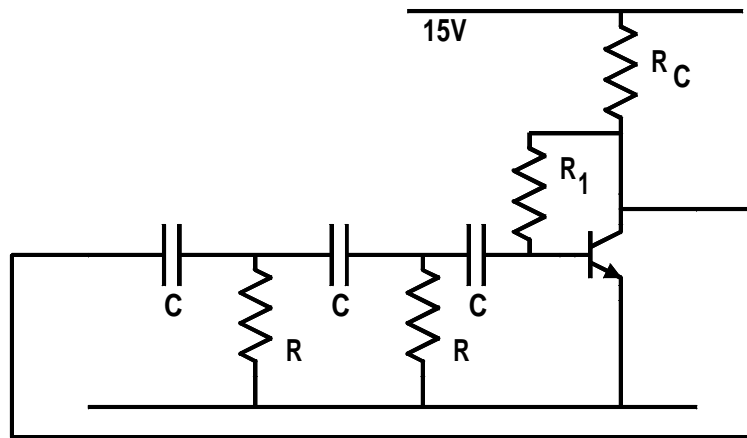

Design a transistor phase shift oscillator for a fixed frequency of  $300\text{Hz}$ .

We then require  $V_C \approx 9\text{V}$  so

$$I_C = \frac{15 - 9}{4700} = 1.28\text{mA}$$

$$\text{then } I_B = \frac{0.00128}{300} = 4.2\mu\text{A}$$

$$\text{which gives } R_B = \frac{9 - 0.7}{4.2\mu\text{A}} = 1.9\text{M}\Omega$$

Given  $f_o = 300\text{Hz}$  then

$$300 \times 2 \times \sqrt{3}CR = 1$$

If we take  $C = 0.01\mu\text{F}$  we get  $R = 980\Omega$ .

Design a Wein bridge oscillator for a fixed frequency of oscillation of  $2000\text{Hz}$  using the circuit in Figure 53.6.

The essential equation is  $f_o = \frac{1}{2\pi CR}$ .

We guess a reasonable value  $C = 0.1\mu F$ .  
which gives  $R = \frac{1}{2\pi f_o C} = 796\Omega$

Determine the value of  $R_B$  and then choose  $R_1$  to get a loop gain of 1, that is, set the gain to at least

$$A_V = 1 + \frac{R_1}{R_B} = 3$$

---