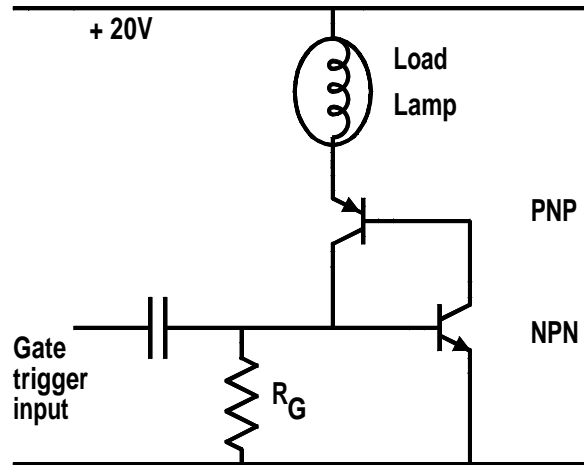


- SCR can conduct in the forward direction.
  - Triac can conduct in either direction
  - UJT is used to give a train of trigger pulses for SCRs and triacs.
  - A diac conducts when the threshold voltage of about  $20V$  is exceeded.
  - In phase angle triggering of triacs, a variable segment of each half waveform of current is passed through the load.
  - In burst fire control, the full power is applied to the load for a variable fraction of the time
-

No power is dissipated in an ideal switch because there is either no voltage drop across the switch or no current in switch.

$$P = V \times I$$

---




A two transistor latch circuit.

No current until triggered.

Then positive feedback gives rapid turn-on and latching action.


---

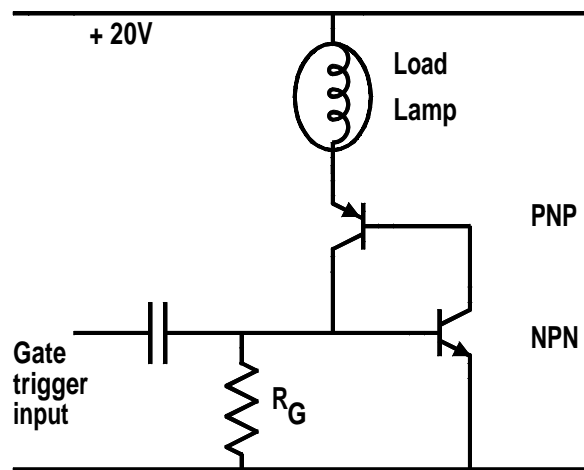

Turned off by turning off power.

Not easy to turn-off electronically.

---

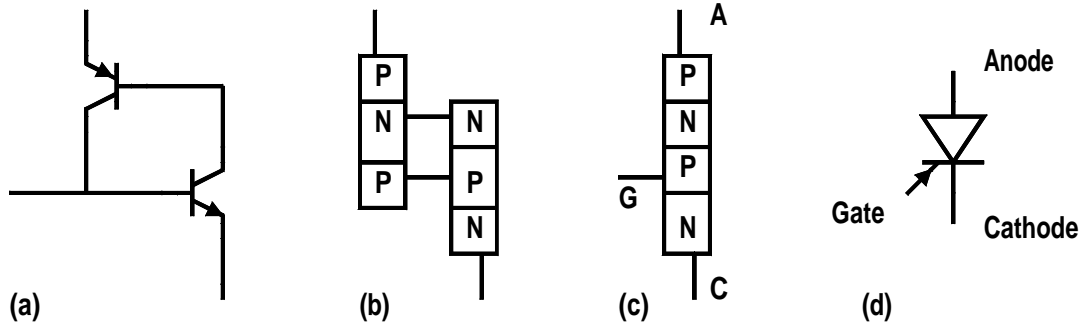

Evolution of a latch circuit to an SCR. Merge layers

Silicon Controlled Rectifier or Thyristor

Holding current


Break Over Voltage

$V_{RRM}$  reverse blocking voltage

Trigger of the order of  $2V$  and  $20mA$  for about  $5\mu s$ .


$\frac{dV}{dt} max$

$I_{T ave}$

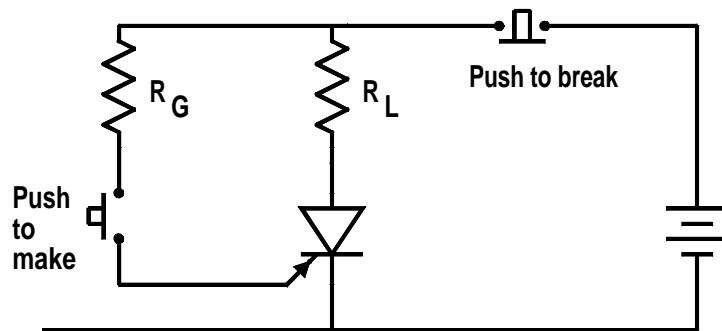


DC triggering of an SCR.

---

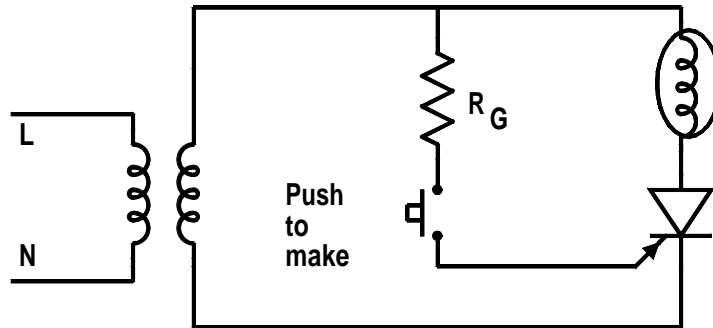


Triggering of an SCR in an AC circuit.

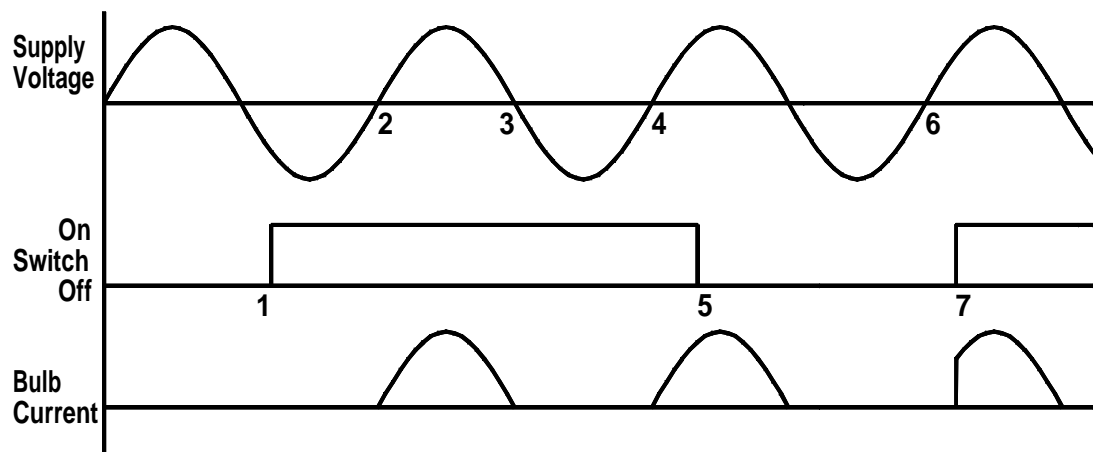


V and I Waveforms in an AC SCR circuit.

Take care with oscilloscope grounds!

---

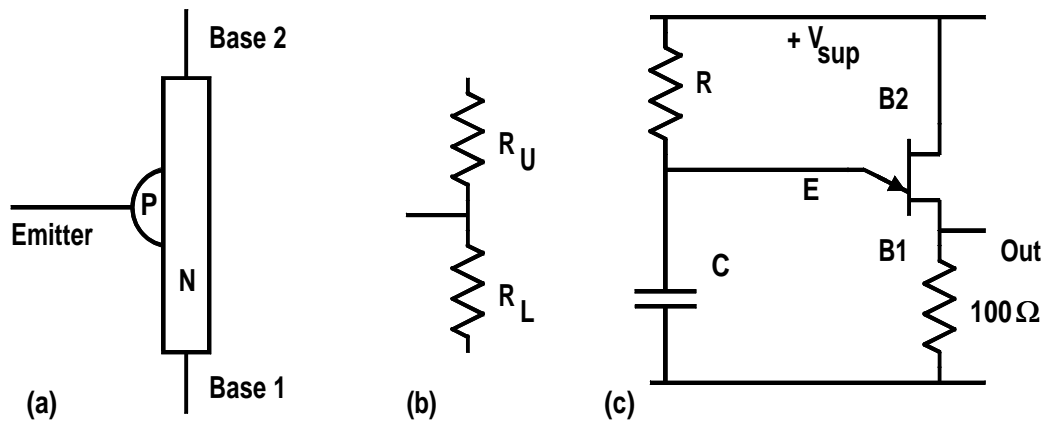


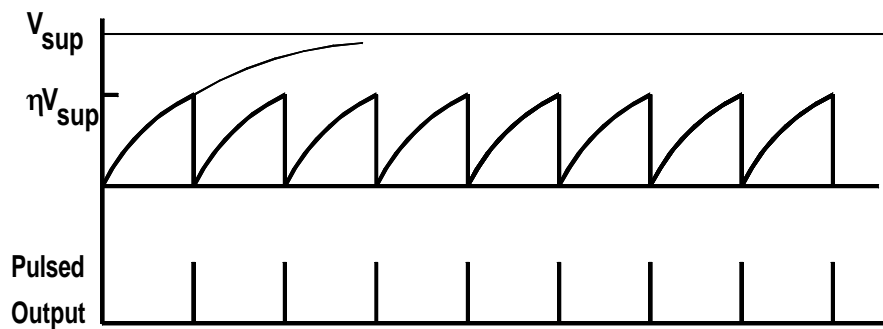Unijunction transistor oscillator circuit.




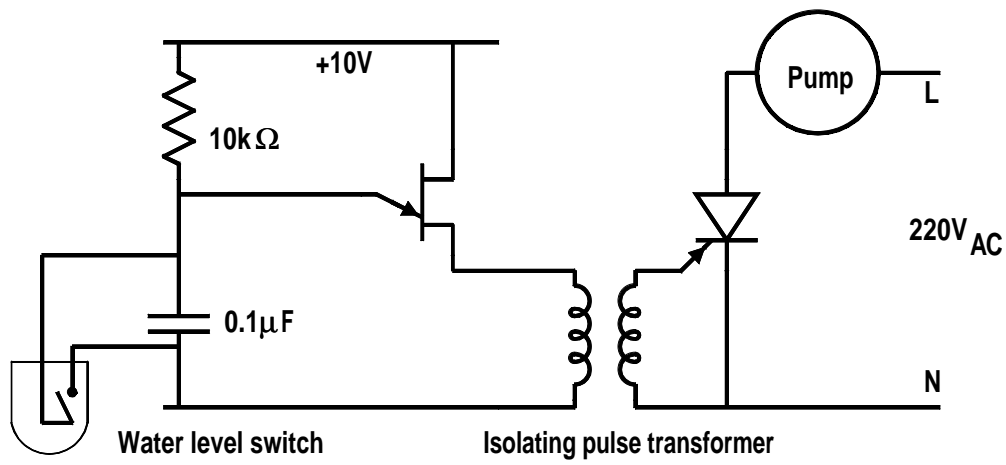
Voltage waveforms in a UJT oscillator circuit.






Use of UJT oscillator for galvanic isolation.

---

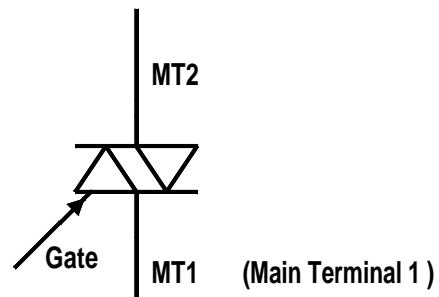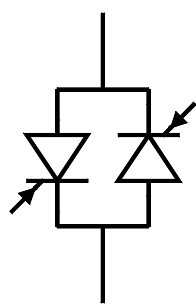

Evolution of two back to back SCR into a TRIAC.


---

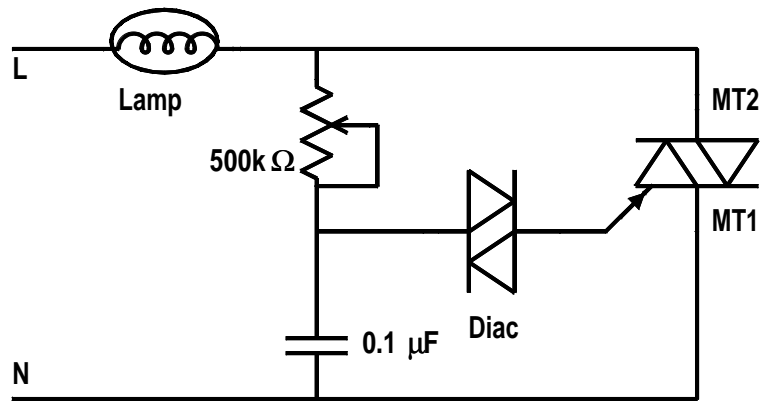

Phase angle triggering of a triac.


Use of a triac allows the implementation of phase control of triggering

---

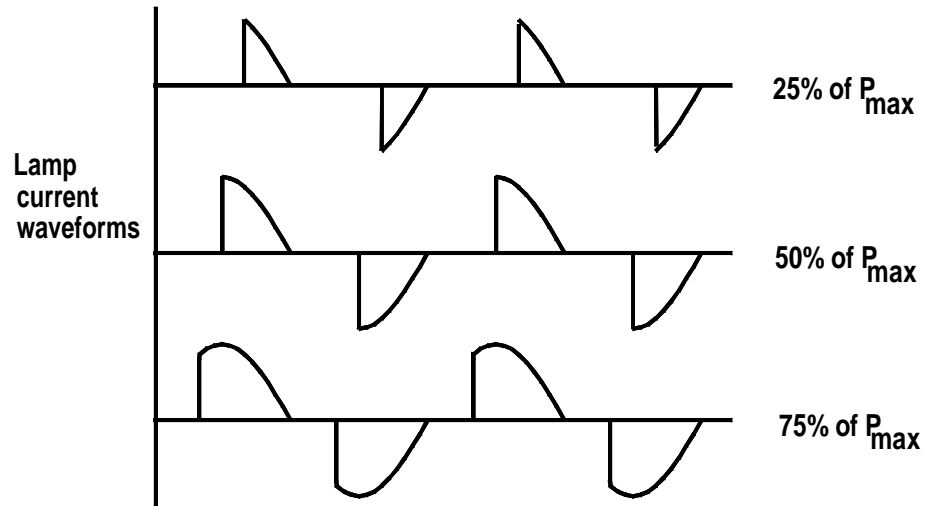

Waveforms in phase angle triggering circuit.

---

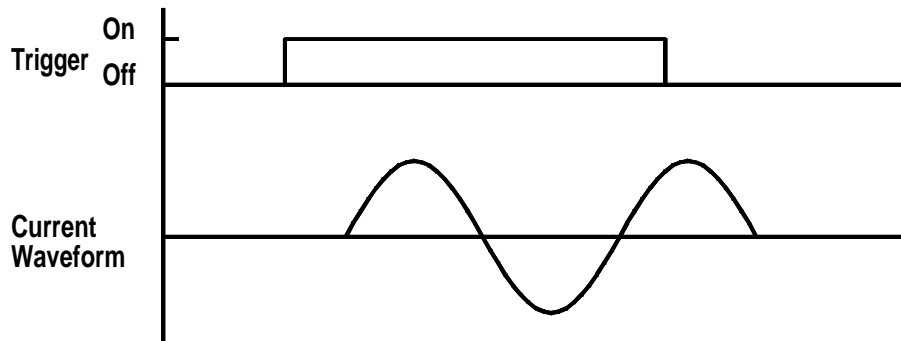

Waveforms in a Zero Volt Switching controller.

When the electrical power supply to heaters, which have a longer time constant than lamps, is to be controlled, a better system is to use a zero volt switch system.

Isolation and reduced interference.

---