
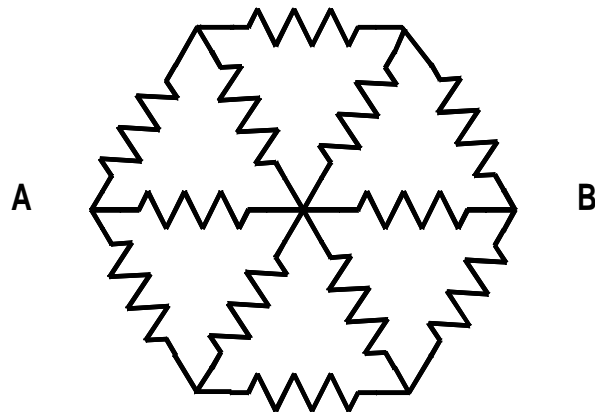


Are these two circuits equivalent?

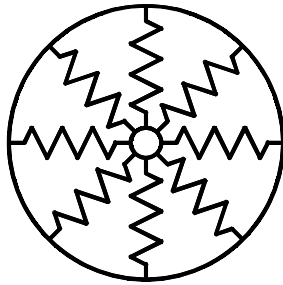
1. Yes
2. No
3. Yes but subject to conditions.
4. What are the conditions




How many lines can be drawn through this circuit which divide the circuit into symmetrical halves?



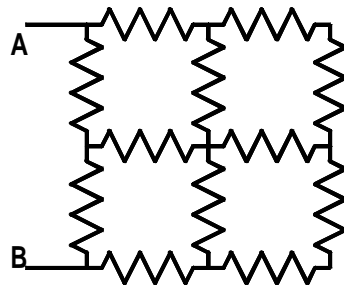How many lines can be drawn through this circuit which divide the circuit into symmetrical halves?



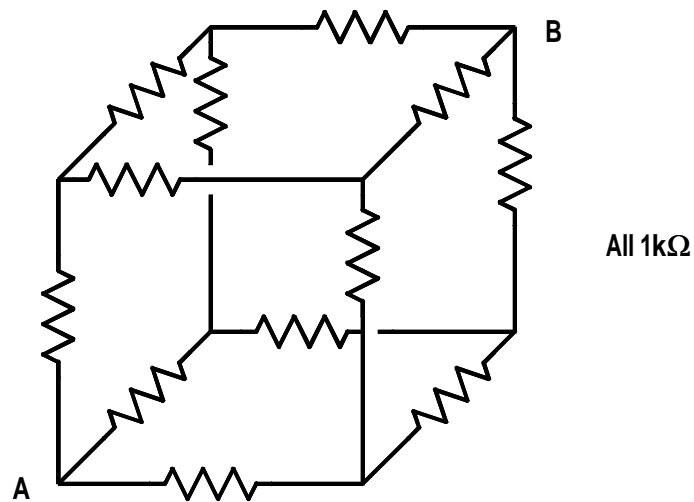How many lines of symmetry are there in this circuit?



How many planes can be drawn through this circuit which divide the circuit into symmetrical halves?