

# DUBLIN CITY UNIVERSITY

**Autumn 2001**

COURSE: APPLIED PHYSICS  
PHYSICS with a LANGUAGE  
YEAR: 2

SEMESTER 1

EXAMINATION: Electronics 1; PS203

EXAMINER: Dr B. Lawless

DURATION: 2 hours

INSTRUCTIONS: Answer 4 parts of Question 1 (50 %)  
and 2 other questions (25 % each)

Do not turn over this page  
until instructed to do so.

**Question 1.** Answer four parts of this question.

- (a) Calculate the Thévenin equivalent of the circuit in Figure 1.

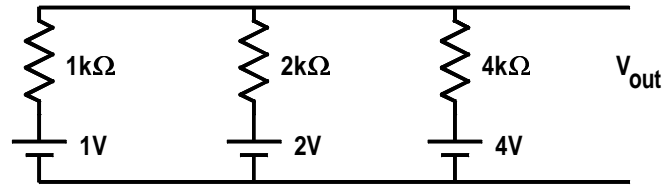


Figure 1: Question 1 (a)

- (b) Calculate the voltage difference between nodes A and B in the circuit of Figure 2.

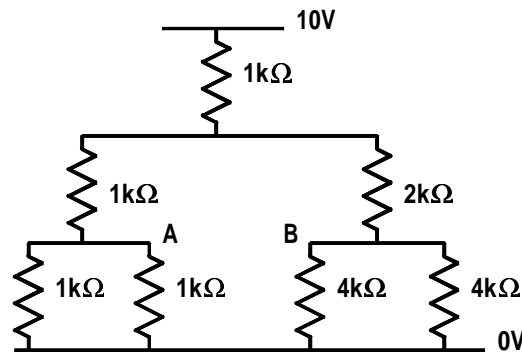


Figure 2: Question 1 (b)

- (c) The three filter circuits A, B and C having the responses shown in Figure 3 are connected in series. Sketch the frequency response of the composite circuit for a frequency range from 10Hz to 1000kHz.

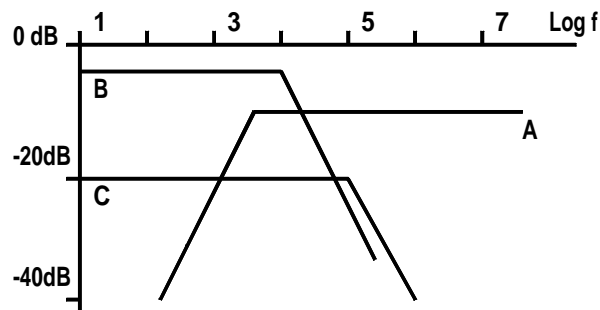


Figure 3: Question 1 (c)

- (d) Calculate the voltages at the nodes A, B, C, D and E in the circuit shown in Figure 4. All the diodes are silicon.

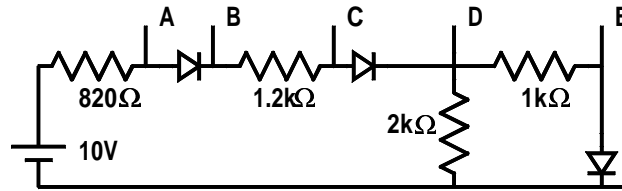


Figure 4: Question 1 (d)

- (e) The collector voltage in the circuit in Figure 5 is measured to be 6.3 V. Calculate the current gain of the transistor.

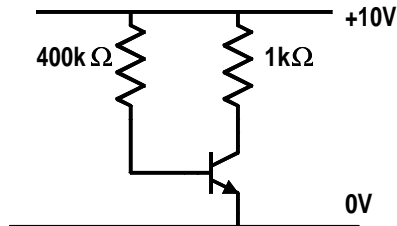


Figure 5: Question 1 (e)

- (f) What is the resonant frequency of the circuit in Figure 6? Sketch the response of the filter as a function of frequency.

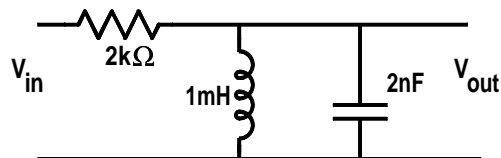


Figure 6: Question 1 (f)

- (g) What current flows in a  $0.1\ \mu\text{F}$  capacitor when a 6 V amplitude sinusoidal signal at a frequency of 400 Hz is applied across the capacitor?

**Question 2.** Calculate the emitter, base and collector voltages for the circuit shown in Figure 7. Calculate the small signal voltage gain of the amplifier. Sketch the waveforms which you would observe with an oscilloscope connected to the emitter, the base and the collector of the circuit when the input voltage is a 3 mV sinusoidal signal at 2 kHz.

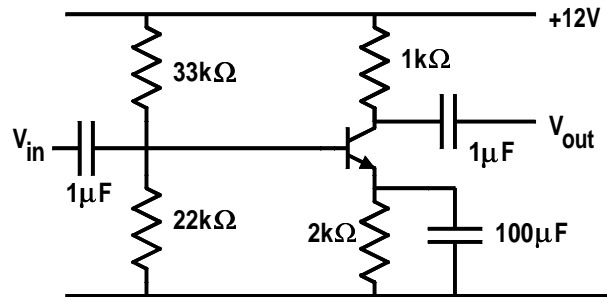


Figure 7: Question 2

**Question 3.** Explain how you would select the component values for the FET amplifier shown in Figure 8 so that the amplifier will have a gain of -5. The JFET has a  $g_m = 2000\mu\text{S}$ ,  $I_{DSS} = 7\text{mA}$  and a  $V_{GS(off)} = 2\text{V}$ .

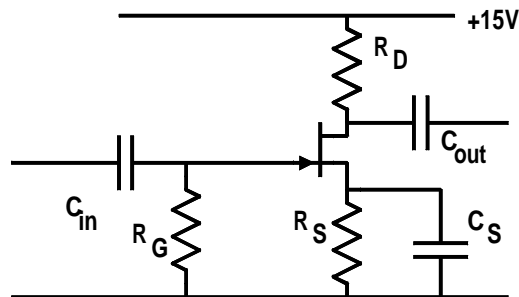


Figure 8: Question 3

**Question 4.** Obtain the equation which relates the output voltage to the input voltages  $V_1$  and  $V_2$  for the circuit shown in Figure 9.

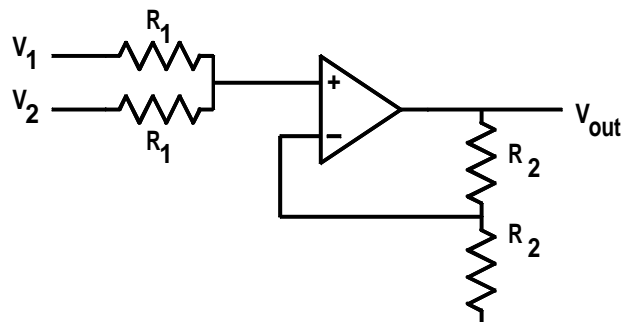


Figure 9: Question 4