

# DUBLIN CITY UNIVERSITY

**Autumn 2002**

COURSE: APPLIED PHYSICS  
PHYSICS with a LANGUAGE

YEAR: 2

SEMESTER 1

EXAMINATION: Electronics 1; PS203

EXAMINER: Dr B. Lawless

DURATION: 2 hours

INSTRUCTIONS: Answer 5 parts of Question 1 (50 %)  
and 2 other questions (25 % each)

Do not turn over this page  
until instructed to do so.

NUMBER OF PAGES 5 (including this cover page.)

**Question 1.** Answer five parts of this question.

- (a) Calculate the required value of resistor,  $R$ , if the input voltage to the circuit in Figure 1 is  $9.3\text{ V}$  and the output voltage is to be  $2.3\text{ V}$ .

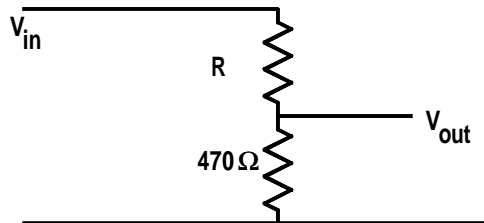


Figure 1: Question 1 (a)

- (b) Calculate the ratio of the output to input voltage for the circuit in Figure 2.  
Convert the calculated voltage ratio to dBs.

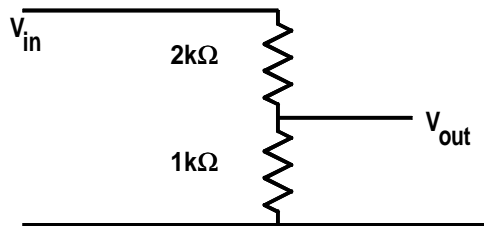


Figure 2: Question 1 (b)

- (c) An alternating current having a sinusoidal waveform at a frequency of  $420\text{ Hz}$  and amplitude  $29\text{ mA}$  flows through a  $250\text{ mH}$  inductor. Calculate the voltage across the inductor.  
Will the voltage be in phase with the current?
- (d) Calculate the complex impedance when  $220\Omega$ ,  $0.3\text{ H}$  and  $1.0\mu\text{F}$  are connected in series and the frequency is  $500\text{ Hz}$ .

- (e) Calculate the amplitude of the output voltage from the circuit in Figure 3 when the input has an amplitude of 3.6 V and the frequency is
- 300 Hz
  - 10 kHz

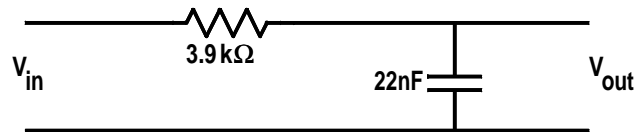


Figure 3: Question 1 (e)

- (f) Calculate the voltage at each of the nodes of the circuit shown in Figure 4. The input voltage is 25 V.

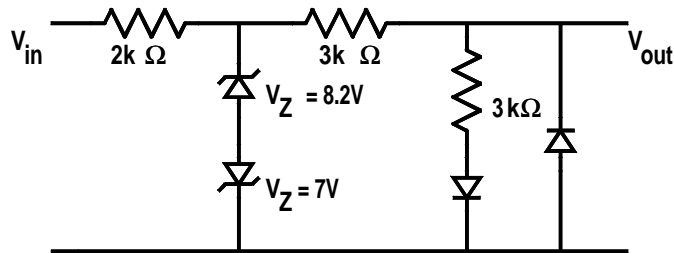


Figure 4: Question 1 (f)

- (g) State Thévenin's theorem.  
Calculate the voltage which will be measured across a  $1\text{ k}\Omega$  resistor which is connected across a battery which has an open circuit voltage of 9.2 V and an internal resistance of  $150\text{ }\Omega$ .
- (h) Calculate the current gain,  $\beta$ , of the transistor in the circuit shown in Figure 5 if a voltage of 4.1 V is measured between the emitter and the collector.

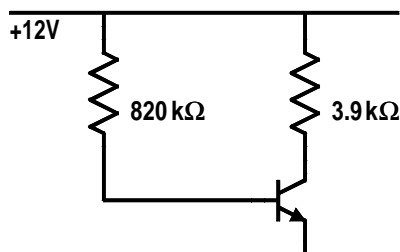


Figure 5: Question 1 (h)

- Question 2.** Calculate the emitter, base and collector voltages for the circuit shown in Figure 6.
- The current gain of the transistor used in the circuit was  $\beta = 180$ .
- Calculate the small signal voltage amplification of the circuit.
- Give a scaled sketch of the output voltage from the circuit when a sinusoidal voltage waveform of  $1.5 \text{ mV}_{pp}$  and frequency  $1 \text{ kHz}$  is applied at the input.

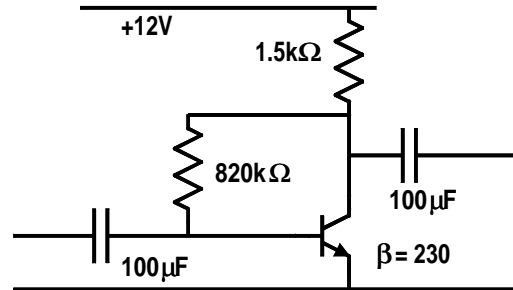


Figure 6: Question 2

- Question 3.** Give an account of the construction and operation of a Junction Field Effect Transistor (JFET) using diagrams where appropriate.
- Explain the meaning of the standard symbols,  $I_{DSS}$ ,  $V_{GS}$ ,  $I_D$  and  $g_m$ .
- A circuit for a small signal JFET amplifier is shown in Figure 7. Explain the operation of the circuit. Give rough values for the voltages which you would expect to measure at the source, gate and drain of the JFET in the circuit.

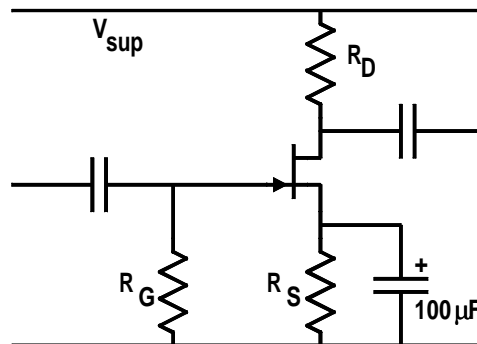


Figure 7: Question 3

- Question 4.** (a) Explain the operation of the inverting amplifier shown in Figure 8. Calculate the voltage gain when  $R_f = 800\text{ k}\Omega$  and  $R_{in} = 7.5\text{ k}\Omega$ .

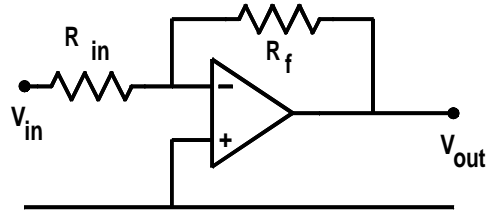


Figure 8: Question 4(a)

- (b) Derive the equation relating the input and the output voltage for the integrator circuit shown in Figure 9.

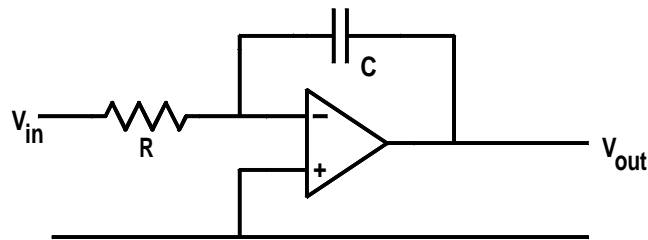


Figure 9: Question 4(b)

- Question 5.** Give an account of the various stages which occur in the process of designing and manufacturing a printed circuit board.  
Give an account of the photolithographic process which occur in the manufacture of transistors and integrated circuits.