

DUBLIN CITY UNIVERSITY

January 2002

COURSE:	APPLIED PHYSICS PHYSICS with a LANGUAGE
YEAR:	2
SEMESTER	1
EXAMINATION:	Electronics 1; PS203
EXAMINER:	Dr B. Lawless
DURATION:	2 hours
INSTRUCTIONS:	Answer 5 parts of Question 1 (50 %) and 2 other questions (25 % each)
	Do not turn over this page until instructed to do so.
NUMBER OF PAGES	8 (including this cover page.)

Question 1. Answer five parts of this question.

- (a) Calculate the voltages which would be measured, with respect to ground, at the nodes A, B, C, D, E, F and G in the circuit in Figure 1.

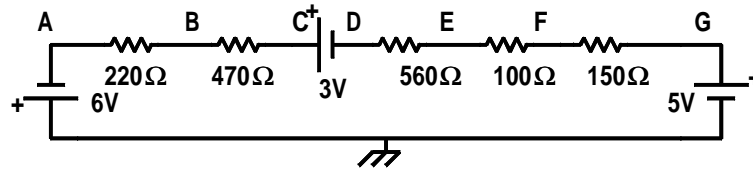


Figure 1: Question 1 (a)

- (b) Calculate the voltages which would be measured, with respect to ground, at the nodes A, B, C and D in the circuit in Figure 2.

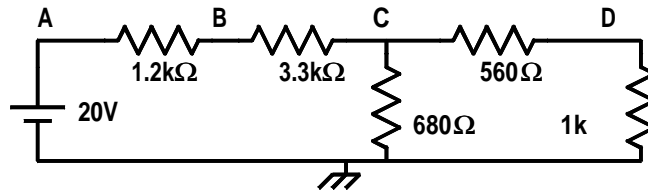


Figure 2: Question 1 (b)

- (c) Calculate the voltages which would be measured, with respect to ground, at the nodes A, B, C, D and E in the circuit in Figure 3.

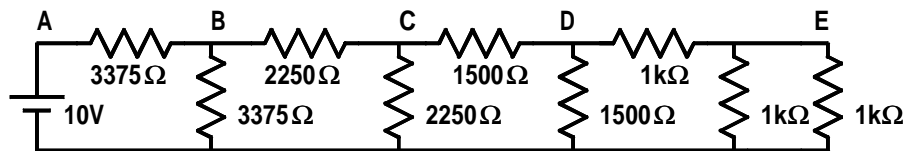


Figure 3: Question 1 (c)

- (d) A sinusoidal voltage waveform of amplitude 15 V is applied across a $1\mu\text{F}$ capacitor. A sensing resistor of value 5Ω is used to display the current waveform on an oscilloscope. Give a scaled sketch of the voltage and current waveforms which would be displayed on the oscilloscope.

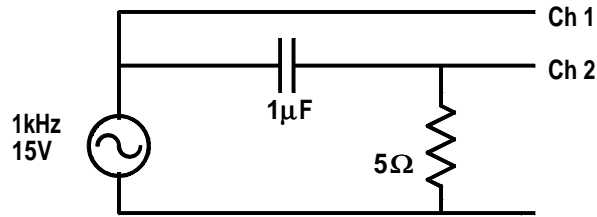


Figure 4: Question 1 (d)

- (e) Give the relationship between the input and output voltages in terms of the impedances Z_1 and Z_2 for the circuit in Figure 5 (a). Calculate the magnitude and relative phase of the current and voltage waveforms for the circuit in Figure 5 (b).

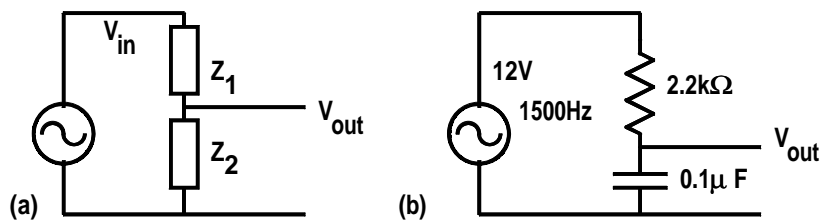


Figure 5: Question 1 (e)

- (f) Sketch the Bode plot for the filter shown in Figure 6.

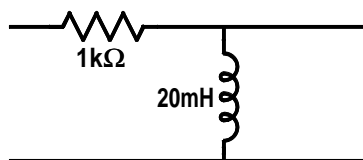


Figure 6: Question 1 (f)

- (g) Calculate the current which flows in the $220\ \Omega$ resistor in the circuit shown in Figure 7.

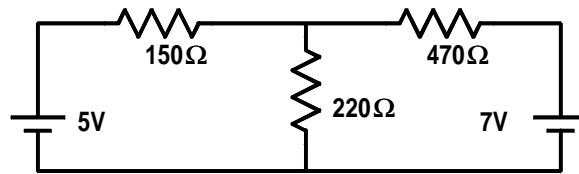


Figure 7: Question 1 (g)

- (h) Calculate the voltages at nodes A, B and C in the circuit shown in Figure 8 for input voltages of -15V , $+10\text{V}$ and $+50\text{V}$.

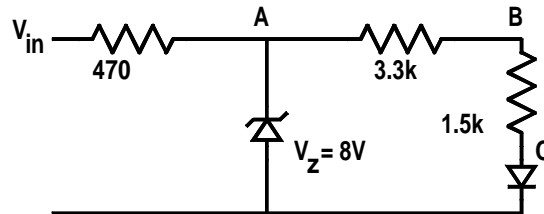


Figure 8: Question 1 (h)

- Question 2.** Calculate the emitter, base and collector voltages and currents for the amplifier shown in Figure 9. Calculate the small signal voltage amplification of the circuit. Give a scaled sketch of the output voltage from the circuit when a sinusoidal voltage waveform of 1.5mV_{pp} and frequency 1kHz is applied at the input. The current gain of the transistor was measured and found to be $\beta = 230$.

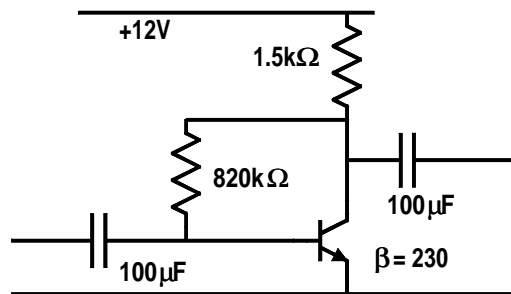


Figure 9: Question 2

Question 3. Calculate the voltage at each of the collectors of the differential amplifier circuit shown in Figure 10.

A DC voltage of 2.5 mV is applied to Input 1 and a sinusoidal voltage of amplitude 1.3 mV and frequency 1 kHz is applied to Input 2. Give a scaled sketch of the voltage which would be observed using an oscilloscope connected to collector 2 (V_{out}) as shown in Figure 10.

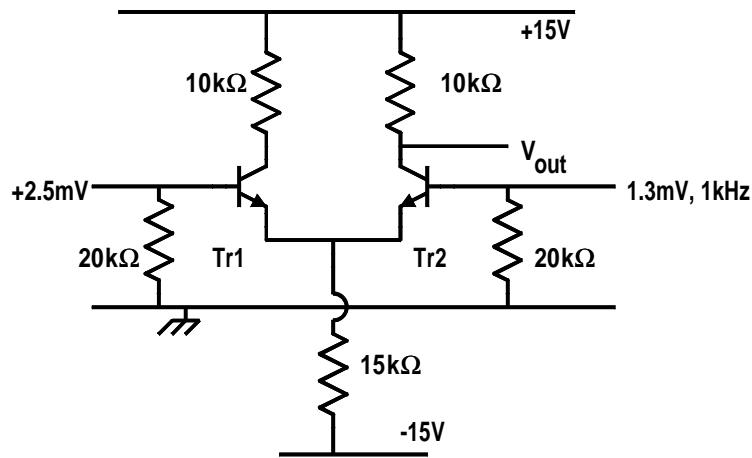


Figure 10: Question 3

Question 4. Explain the operation of the Inverting Adder circuit shown in Figure 11. Derive the equation which relates the output voltage to the input voltages V_1 , V_2 and V_3 .

Give a scaled sketch of the output voltage waveform which would be observed on an oscilloscope when $V_1 = +0.2$ V, $V_2 = -1.5$ V and $V_3 = 2.0 \sin(2\pi 500t)$ V.

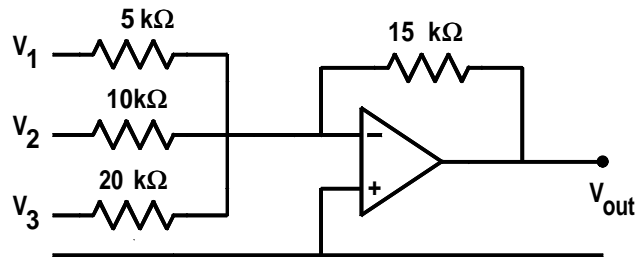


Figure 11: Question 4

Question 5. Explain how the circuits in Figure 12 (a) and (b) allow the values of I_{DSS} and $V_{GS(off)}$ for a JFET to be easily measured.

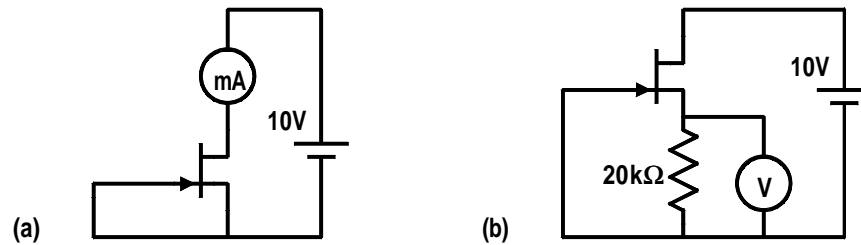


Figure 12: Question 5

Calculate the component values if the amplifier shown in Figure 13 is to have a gain of -5.

The JFET used has $I_{DSS} = 7.5 \text{ mA}$ and $V_{GS(off)} = 3.5 \text{ V}$.

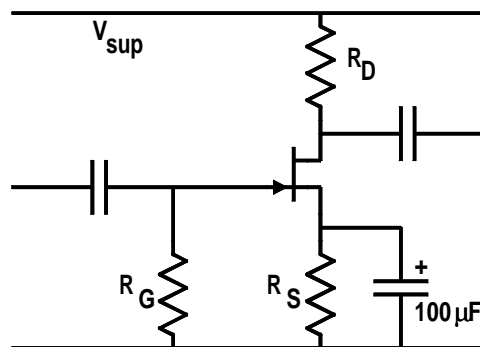


Figure 13: Question 5