

$$\begin{aligned}
 V &= I \times R \\
 R_{series} &= R_1 + R_2 + R_3 + \dots \\
 \frac{1}{R_{parallel}} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \\
 C_{parallel} &= C_1 + C_2 + C_3 + \dots \\
 \text{Power } P &= V \times I = I^2 \times R = \frac{V^2}{R} \text{ watts} \\
 \text{Power ratio} &= 10 \log \left( \frac{P_{out}}{P_{in}} \right) = 20 \log \left( \frac{V_{out}}{V_{in}} \right) \\
 \omega &= 2\pi f \\
 T &= \frac{1}{f} \\
 V &= V_0 \sin(2\pi f t + \phi) \\
 I &= I_0 \sin(2\pi f t + \phi) \\
 V_{Amplitude} &= 1.4 \times V_{RMS} \\
 V_{Peak-to-Peak} &= 2 \times V_{Amplitude} \\
 \text{Air core } L(\text{nH}) &= \frac{N^2 d^2}{0.46d + 1.02b} \\
 \text{Ferrite core } L(\text{nH}) &= N^2 A_L \\
 Z_R &= R \text{ for resistance} \\
 Z_C &= \frac{1}{j\omega C} \text{ for capacitor} \\
 Z_L &= j\omega L \text{ for inductor} \\
 V &= ZI \\
 &= |Z| e^{j\phi} I \\
 \text{or } V_0 e^{j\omega t} &= |Z| I_0 e^{j(\omega t + \phi)} \\
 Z &= R + jX
 \end{aligned}$$

where  $R$  is the resistance,  $X$  is the reactance.  
Generalized potential divider:

$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = |A| e^{j\phi}$$

Then  $|A|$  = attenuation and  $\phi$  = phase shift

$$|c| = |a + jb| = \sqrt{a^2 + b^2} \quad \tan \phi = \frac{b}{a}$$

$$\left| \frac{1}{c} \right| = \left| \frac{1}{a + jb} \right| = \frac{1}{\sqrt{a^2 + b^2}} \quad \tan \phi = \frac{-b}{a}$$

$$f_{corner} = \frac{1}{2\pi CR} \quad \text{or} \quad \frac{R}{2\pi L}$$

Thévenin's theorem  $R_{out} = \frac{V_{out \text{ open circuit}}}{I_{out \text{ short circuit}}}$

Principle of superposition: Replace voltage sources by short circuits and current sources by open circuits.

Semiconductor equation:

$$n \times p = n_i^2 = \text{constant for constant } T$$

Current through a pn diode junction is:

$$\begin{aligned}
 I &= I_0 \left( \exp \left( \frac{eV}{kT} \right) - 1 \right) \\
 &\approx I_0 \exp \left( \frac{V}{25 \text{ mV}} \right) \\
 \frac{kT}{e} &= 25 \text{ mV}
 \end{aligned}$$

Voltage across diode is:

$$V = V_k + I \times R_B$$

where  $V_k = 0.7 \text{ V}$  for Si,  $0.3 \text{ V}$  for Ge.

$$R_{dyn} = \frac{dV}{dI} = \frac{25 \text{ mV}}{I}$$

Ripple voltage of rectified and smoothed AC is:

$$\frac{I_{out}}{2 \times f \times C}$$

Zener diode conducts in reverse bias when the voltage is greater than the Zener voltage for the diode.

For a bipolar transistor:

$$\begin{aligned}
 I_C &= \beta \times I_B \\
 I_C &\approx I_E \\
 V_{BE} &\approx 0.7 \text{ V}
 \end{aligned}$$

Basic equation for transistor bias circuits is:

Voltage supply = Sum of individual voltage drops

Common emitter amplifier amplification:

$$\begin{aligned}
 A_V &= -\frac{I_E}{25 \text{ mV}} \times R_C \\
 R_{in} &= \beta \times \frac{25 \text{ mV}}{I_E}
 \end{aligned}$$

A JFET is specified by:

$$\begin{aligned}
 V_{GS(off)} &= \text{Gate to source cutoff Voltage} \\
 I_{DSS} &= \text{Drain saturation current} \\
 g_m &= \frac{dI_D}{dV_{GS}} = \text{Mutual conductance} \\
 I_D &= I_{DSS} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2
 \end{aligned}$$

An enhancement mode MOSFET is specified by:

$$I_D = k(V_{GS} - V_{GS(th)})^2$$

For a JFET common source amplifier select:

- $R_S = \left| \frac{V_{GS(off)}}{I_{DSS}} \right|$
- Then  $V_{GS} \approx 0.4 \times V_{GS(off)}$
- and  $I_D \approx 0.4 \times I_{DSS}$
- $A_V = -g_m \times R_D$

$$g_m = \frac{dI_D}{dV_{GS}} = -2 \frac{I_{DSS}}{V_{GS(off)}} \left( 1 - \frac{V_{GS}}{V_{GS(off)}} \right)$$

For op-amps used in linear region:

- **Rule 1.** The voltage difference between the inverting and noninverting inputs is approximately zero.
- **Rule 2.** No current flows into the input terminals of the op-amp.
- The gain of an inverting amplifier is:

$$A_V = -\frac{R_f}{R_{in}}$$

- The gain of a noninverting amplifier is:

$$A_V = 1 + \frac{R_1}{R_2}$$

- $A_V = \frac{1}{\beta} = \frac{1}{\text{Feedback fraction}}$
- The output from an inverting adder is:

$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots \right)$$

- Output of current to voltage converter is:

$$V_{out} = -I \times R_f$$

- A bridge is in balance when:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

- For a differential amplifier:

$$V_{out} = \frac{R_2}{R_1} \times (V_2 - V_1)$$

- For a differentiator:

$$V_{out} = -C R_f \frac{dV_{in}}{dt}$$

- For an integrator:

$$V_{out} = -\frac{1}{CR} \int V_{in} dt$$

If a component characteristic is  $I = f(V)$  then:

- Putting the component in place of the input resistor of an inverting amplifier gives the forward function:

$$V_{out} = -R \times f(V_{in})$$

- Putting the component in place of the feedback resistor of an inverting amplifier gives the inverse function:

$$V_{out} = -f^{-1} \left( \frac{V_{in}}{R} \right)$$

Frequency response of a 741 op-amp:

- Has a corner at 10Hz and 100 dB.
- Open loop gain decreases by 20 dB per decade above 10 Hz

Noise in bandwidth  $B$  has units of:

$$\text{Volts per } \sqrt{\text{Hz}} \quad \text{or} \quad \text{Amps per } \sqrt{\text{Hz}}$$

- Thermal noise from a resistor,  $R$ , at temperature  $T$  within a bandwidth  $B$  is:

$$V_{noise} = \sqrt{4kTRB}$$

- The shot noise is:

$$I_{noise} = \sqrt{2eIB}$$

- Flicker noise spectrum varies as

$$\frac{1}{f} = \frac{1}{\text{Frequency}}$$

For a 555 Timer IC:

$$T_1 = 0.7(R_A + R_B)C \quad \text{and} \quad T_2 = 0.7R_B C$$

Sinusoidal voltage waveforms are obtained by using an amplifier with:

- Positive feedback,
- Loop gain of 1
- Frequency selective feedback network.

An  $R-2R$  ladder gives an output:

$$V_{out} = -R_f \frac{V_{ref}}{4R} \left( S_0 + \frac{S_1}{2} + \frac{S_2}{4} + \frac{S_3}{8} + \dots \right)$$