

Unit 15 Generalized potential divider

- Resistive or reactive components used in potential dividers give:

$$V_{out} = \frac{Z_2}{Z_1 + Z_2} V_{in}$$

- When the term $\frac{Z_2}{Z_1 + Z_2}$ is put into the form $|A| e^{j\phi}$ then $|A|$ is the attenuation of the potential divider and ϕ is the phase shift.
-

There are two results from complex algebra which we will use extensively and which you may need to follow up in your mathematics textbook.

When a complex number, c , is in the form $c = a + jb$, the modulus and the phase angle for c and $\frac{1}{c}$ are given by:

$$|c| = |a + jb| = \sqrt{a^2 + b^2} \quad \text{and} \quad \tan \phi = \frac{b}{a}$$

$$\left| \frac{1}{c} \right| = \left| \frac{1}{a + jb} \right| = \frac{1}{\sqrt{a^2 + b^2}} \quad \text{and} \quad \tan \phi = \frac{-b}{a}$$

The resistors in the potential divider discussed in Unit 4 can be replaced by any combination of resistors, capacitors or inductors in series or parallel. A resultant impedance can then be calculated for each half of the potential divider. The current in each of the two impedances is given by $\frac{V_{in}}{Z_1 + Z_2}$. This current flowing through Z_2 gives an output voltage $Z_2 I$.

The ratio of output to input voltage is then:

$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

but since Z_1 and Z_2 are complex then $\frac{Z_2}{Z_1 + Z_2}$ is usually also complex and has a magnitude less than 1.

If we express $\frac{Z_2}{Z_1 + Z_2}$ in the form $|A| e^{j\phi}$ then $|A|$ gives the attenuation of the potential divider and ϕ gives the phase shift in radians.

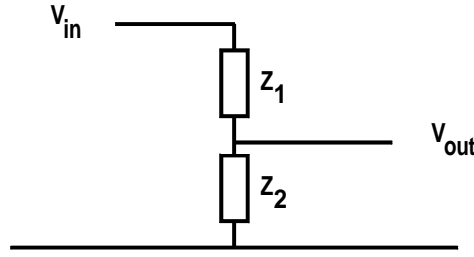


Figure 15.1: Generalized potential divider.

15.1 Example

15.1 Calculate the attenuation and phase shift in the RC network in Figure 15.2 where $R = 2.2 \text{ k}\Omega$, $C = 0.1 \text{ }\mu\text{F}$ and the frequency is 1.5 kHz .

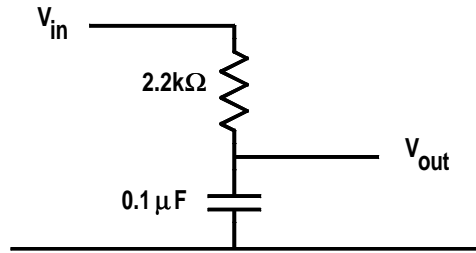


Figure 15.2: Example 15.1.

The network response is given by:

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{Z_2}{Z_1 + Z_2} \\ &= \frac{\frac{1}{j2\pi fC}}{R + \frac{1}{j2\pi fC}} \\ &= \frac{1}{1 + j2\pi fCR} \end{aligned}$$

$$\begin{aligned} \text{First calculate } \tan \phi &= -2\pi fCR \\ &= -2\pi 1500 \times 0.1 \times 10^{-6} \times 2200 \\ &= -2.07 \end{aligned}$$

$$\begin{aligned} \text{So that } \phi &= \tan^{-1}(-2.07) \\ &= -1.12 \text{ rad or } -64.3^\circ \end{aligned}$$

$$\begin{aligned} \text{and the attenuation is } \left| \frac{V_{out}}{V_{in}} \right| &= \frac{1}{\sqrt{1 + \tan^2 \phi}} = \frac{1}{\sqrt{1 + 2.07^2}} \\ &= 0.435 = 20 \log 0.435 \text{ dB} = -7.23 \text{ dB} \end{aligned}$$

If this circuit is constructed and the input and output waveforms are displayed on an oscilloscope then a trace similar to that in Figure 15.3 should be obtained.

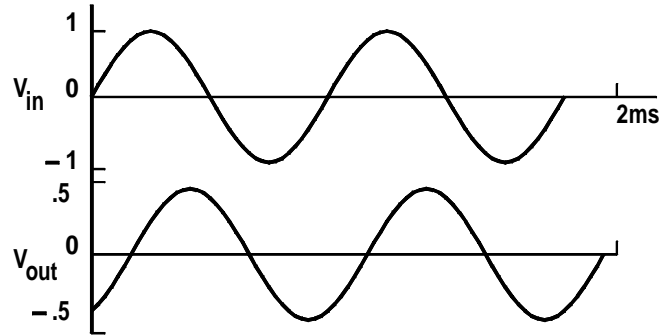


Figure 15.3: Input and output voltage waveforms for Example 15.1.

In the calculations we obtained a phase shift of -1.12 radians. In the oscilloscope diagram it can be seen that the output waveform is displaced to the right by 1.12 radians or 64° relative to the input voltage waveform. So we obtain the useful rule that:

- If the phase shift is positive then the output waveform is shifted to the left and is said to lead the input waveform.
- If the phase shift is negative then the output waveform is shifted to the right and is said to lag the input waveform.

15.2 Problems

- 15.1 Write down the expression for the output voltage waveform in Example 15.1 shown in Figure 15.3.
- 15.2 Calculate the attenuation and phase shift for the RC circuit shown in Figure 15.4 when $f = 500$ Hz, $C = 22$ nF and $R = 10$ k Ω . Sketch the input and output voltage waveforms showing the amplitude and phase of the signals. Assume that the input signal is $1V_{pp}$.

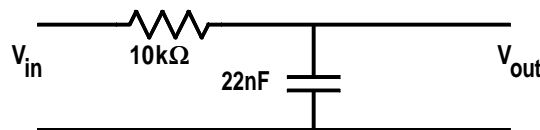


Figure 15.4: Problem 15.2.

- 15.3 Calculate the attenuation and phase shift for the CR circuit shown in Figure 15.5 when $f = 1.5 \text{ kHz}$, $C = 0.1 \mu\text{F}$ and $R = 1.2 \text{ k}\Omega$. Sketch the input and output voltage waveforms showing the amplitude and phase of the signals. Assume that the input signal is of amplitude 1 V .



Figure 15.5: Problem 15.3.

- 15.4 Calculate the attenuation and phase shift for the LR circuit shown in Figure 15.6 when $f = 7 \text{ kHz}$, $L = 10 \text{ mH}$ and $R = 680 \Omega$. Sketch the input and output voltage waveforms showing the amplitude and phase of the signals. Assume that the input signal is 1 V_{pp} .

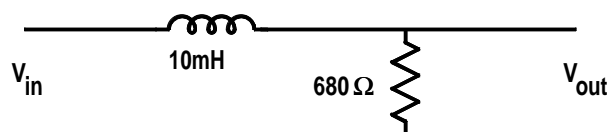


Figure 15.6: Problem 15.4.

- 15.5 Calculate the attenuation and phase shift for the RL circuit shown in Figure 15.7 when $f = 60 \text{ kHz}$, $L = 1 \text{ mH}$ and $R = 470 \Omega$. Sketch the input and output voltage waveforms showing the amplitude and phase of the signals. Assume that the input signal is 1 V_{pp} .

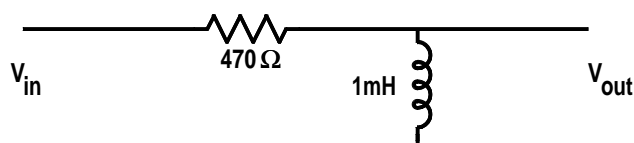


Figure 15.7: Problem 15.5.

- 15.6 Calculate the frequency for which the attenuation is 3 dB for the circuit in Figure 15.8. Calculate the phase shift in degrees at this frequency.

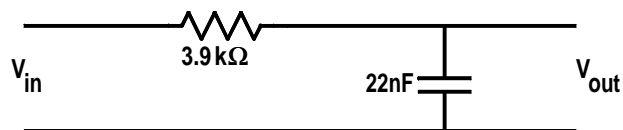


Figure 15.8: Problem 15.6.

- 15.7 Show that the bridge circuit in Figure 15.9 will be in balance, that is $V_A = V_B$, when $R_X = \frac{R_3 \times R_2}{R_1}$.

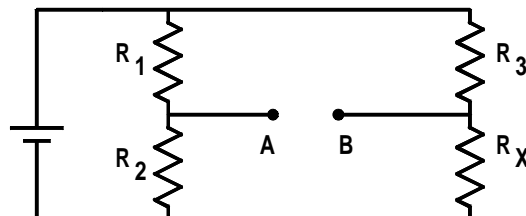


Figure 15.9: Problem 15.7.

- 15.8 Show that the Simple bridge in Figure 15.10 will be in balance when:

$$R_X = \frac{R_2 \times R_3}{R_1} \quad \text{and} \quad C_X = \frac{R_1}{R_3} \times C_2$$

Does the balance depend on the frequency of the voltage across the bridge? Note that the real and complex parts of the impedance equation must balance separately.

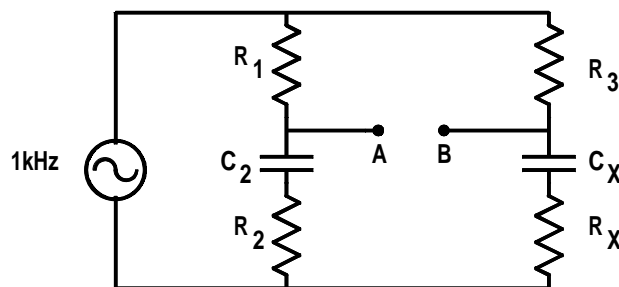


Figure 15.10: Problem 15.8.